
EEE3571 Electronic Engineering I

Lecture 7: Field Effect Transistors DC Biasing and Small-signal Analysis



May 2023

daliso.banda@unza.zm

References

Our main reference text books in this course are

- [1] Neil S., [Electronics: A Systems Approach](#), 4th edition, 2009, Pearson Education Limited, ISBN 978-0-273-71918-2.
- [2] Boylestad R. L., Nashelsky L., [Electronic Devices and Circuit Theory](#), 11th Ed, 2013, Prentice-Hall, ISBN 978-0-13-262226-4.
- [3] Smith R. J., Dorf R. C., [Circuits Devices and Systems](#), 5th Ed., 2004, John Wiley, ISBN ISBN 9971-51-172-X.

However, feel free to use pretty much any additional text which you might find relevant to our course.

Learning Objectives

At the end of this, you ought to:

- 1) Be able to compute the bias points of JFETs for the following configurations:
 - 1) Fixed bias and
 - 2) Voltage-divider configuration.
- 2) Be able to compute the bias points of E-MOSFETs for the Voltage divider configuration.
- 3) Be introduced to the small-signal model for E-MOSFETS and thus be able to compute ac-parameters for a potential-divider bias based E-MOSFET amplifier.

FET Equations Summary

JFET:

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$I_D = I_{DSS} |_{V_{GS}=0 \text{ V}}, \quad I_D = 0 \text{ mA} |_{V_{GS}=V_P}, \quad I_D = \frac{I_{DSS}}{4} |_{V_{GS}=V_P/2}, \quad V_{GS} \cong 0.3 V_P |_{I_D=I_{DSS}/2}$$

$$V_{GS} = V_P \left(1 - \sqrt{\frac{I_D}{I_{DSS}}} \right)$$

$$P_D = V_{DS} I_D$$


$$r_d = \frac{r_o}{(1 - V_{GS}/V_P)^2}$$

MOSFET (enhancement):

$$I_D = k(V_{GS} - V_T)^2$$

$$k = \frac{I_{D(\text{on})}}{(V_{GS(\text{on})} - V_T)^2}$$

JFET fixed-bias configuration

 

JFET fixed-bias configuration

EXAMPLE 7.1 Determine the following for the network of Fig. 7.6:

- V_{GSQ} .
- I_{DQ} .
- V_{DS} .
- V_D .
- V_G .
- V_S .

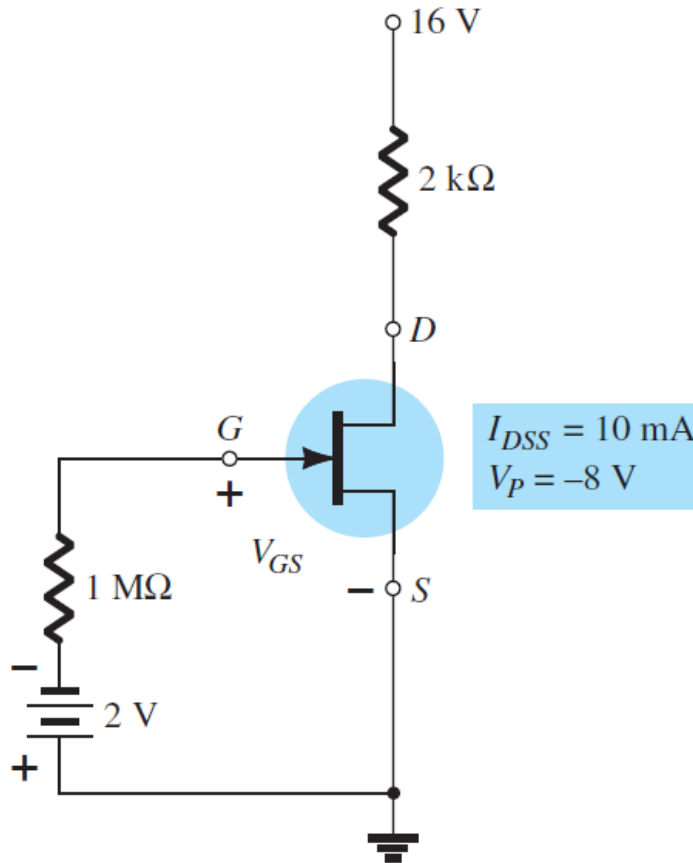


FIG. 7.6

Example 7.1.

JFET fixed-bias configuration

Solution:

Mathematical Approach

a. $V_{GS_Q} = -V_{GG} = -2 \text{ V}$


b.
$$I_{D_Q} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 = 10 \text{ mA} \left(1 - \frac{-2 \text{ V}}{-8 \text{ V}} \right)^2$$
$$= 10 \text{ mA} (1 - 0.25)^2 = 10 \text{ mA} (0.75)^2 = 10 \text{ mA} (0.5625)$$
$$= \mathbf{5.625 \text{ mA}}$$

c.
$$V_{DS} = V_{DD} - I_D R_D = 16 \text{ V} - (5.625 \text{ mA})(2 \text{ k}\Omega)$$
$$= 16 \text{ V} - 11.25 \text{ V} = \mathbf{4.75 \text{ V}}$$

d. $V_D = V_{DS} = \mathbf{4.75 \text{ V}}$

e. $V_G = V_{GS} = -2 \text{ V}$


f. $V_S = \mathbf{0 \text{ V}}$

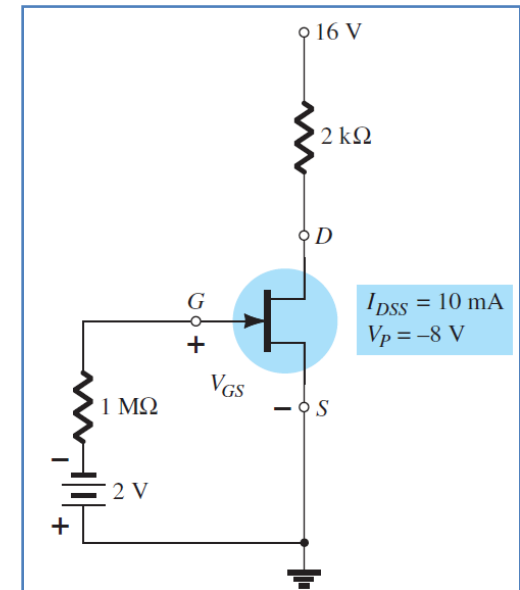

JFET fixed-bias configuration

Graphical Approach

Plot using Shockley's equation.

 

JFET fixed-bias configuration

Graphical Approach

a. Therefore,

$$V_{GS_Q} = -V_{GG} = -2 \text{ V}$$

b. $I_{D_Q} = 5.6 \text{ mA}$

c. $V_{DS} = V_{DD} - I_D R_D = 16 \text{ V} - (5.6 \text{ mA})(2 \text{ k}\Omega)$
 $= 16 \text{ V} - 11.2 \text{ V} = 4.8 \text{ V}$

d. $V_D = V_{DS} = 4.8 \text{ V}$

e. $V_G = V_{GS} = -2 \text{ V}$


f. $V_S = 0 \text{ V}$

The results clearly confirm the fact that the mathematical and graphical approaches generate solutions that are quite close.

JFET Voltage-divider biasing

 EXAMPLE 7.4 Determine the following for the network of Fig. 7.21:

- I_{DQ} and V_{GSQ} .
- V_D .
- V_S .
- V_{DS} .
- V_{DG} .



JFET Voltage-divider biasing

- a. For the transfer characteristics, if $I_D = I_{DSS}/4 = 8 \text{ mA}/4 = 2 \text{ mA}$, then $V_{GS} = V_P/2 = -4 \text{ V}/2 = -2 \text{ V}$. The resulting curve representing Shockley's equation appears in Fig. 7.22. The network equation is defined by

$$\begin{aligned}V_G &= \frac{R_2 V_{DD}}{R_1 + R_2} \\&= \frac{(270 \text{ k}\Omega)(16 \text{ V})}{2.1 \text{ M}\Omega + 0.27 \text{ M}\Omega} \\&= 1.82 \text{ V}\end{aligned}$$

and

$$\begin{aligned}V_{GS} &= V_G - I_D R_S \\&= 1.82 \text{ V} - I_D(1.5 \text{ k}\Omega)\end{aligned}$$

When $I_D = 0 \text{ mA}$,


$$V_{GS} = +1.82 \text{ V}$$

When $V_{GS} = 0 \text{ V}$,

$$I_D = \frac{1.82 \text{ V}}{1.5 \text{ k}\Omega} = 1.21 \text{ mA}$$

We then plot the input characteristics and the straight line from KVL on the input on the same axis to determine the intersection point.

JFET Voltage-divider biasing

 

JFET Voltage-divider biasing

$$\begin{aligned} \text{b. } V_D &= V_{DD} - I_D R_D \\ &= 16 \text{ V} - (2.4 \text{ mA})(2.4 \text{ k}\Omega) \\ &= \mathbf{10.24 \text{ V}} \end{aligned}$$

$$\begin{aligned} \text{c. } V_S &= I_D R_S = (2.4 \text{ mA})(1.5 \text{ k}\Omega) \\ &= \mathbf{3.6 \text{ V}} \end{aligned}$$

$$\begin{aligned} \text{d. } V_{DS} &= V_{DD} - I_D(R_D + R_S) \\ &= 16 \text{ V} - (2.4 \text{ mA})(2.4 \text{ k}\Omega + 1.5 \text{ k}\Omega) \\ &= \mathbf{6.64 \text{ V}} \end{aligned}$$


$$\begin{aligned} \text{or } V_{DS} &= V_D - V_S = 10.24 \text{ V} - 3.6 \text{ V} \\ &= \mathbf{6.64 \text{ V}} \end{aligned}$$

Biasing of Depletion-Type MOSFETs

- ❑ Generally the same procedure used to determine the operating point of JFETs is used for depletion-type MOSFETS consequently they will not be covered here.
- ❑ Kindly see examples and questions in the prescribed textbook.

Voltage-divider biasing for Enhancement-Type MOSFETs

 - ❑ The transfer characteristics of the enhancement-type MOSFET are quite different from those encountered for the JFET and depletion-type MOSFETs,
- ❑ The transfer function is given by:



Voltage-divider biasing for Enhancement-Type MOSFETs

EXAMPLE 7.11 Determine I_{DQ} , V_{GSQ} , and V_{DS} for the network of Fig. 7.44.

 


FIG. 7.44

Voltage-divider biasing for Enhancement-Type MOSFETs

EXAMPLE 7.11 Determine I_{DQ} , V_{GSQ} , and V_{DS} for the network of Fig. 7.44.

 


FIG. 7.44

Network

$$V_G = \frac{R_2 V_{DD}}{R_1 + R_2} = \frac{(18\text{ M}\Omega)(40\text{ V})}{22\text{ M}\Omega + 18\text{ M}\Omega} = 18\text{ V}$$

$$V_{GS} = V_G - I_D R_S = 18\text{ V} - I_D(0.82\text{ k}\Omega)$$

When $I_D = 0\text{ mA}$,

$$V_{GS} = 18\text{ V} - (0\text{ mA})(0.82\text{ k}\Omega) = 18\text{ V}$$

When $V_{GS} = 0\text{ V}$,

$$V_{GS} = 18\text{ V} - I_D(0.82\text{ k}\Omega)$$

$$0 = 18\text{ V} - I_D(0.82\text{ k}\Omega)$$

$$I_D = \frac{18\text{ V}}{0.82\text{ k}\Omega} = 21.95\text{ mA}$$

Voltage-divider biasing for Enhancement-Type MOSFETs

EXAMPLE 7.11 Determine I_{DQ} , V_{GSQ} , and V_{DS} for the network of Fig. 7.44.

 


FIG. 7.44

Device

$$V_{GS(\text{Th})} = 5 \text{ V}, \quad I_{D(\text{on})} = 3 \text{ mA with } V_{GS(\text{on})} = 10 \text{ V}$$

2N4351
 $V_{GS(\text{Th})} = 5 \text{ V}$
 $I_{D(\text{on})} = 3 \text{ mA}$
 at $V_{GS(\text{on})} = 10 \text{ V}$


$$k = \frac{I_{D(\text{on})}}{(V_{GS(\text{on})} - V_{GS(\text{Th})})^2} = \frac{3 \text{ mA}}{(10 \text{ V} - 5 \text{ V})^2} = 0.12 \times 10^{-3} \text{ A/V}^2$$

$$I_D = k(V_{GS} - V_{GS(\text{Th})})^2 = 0.12 \times 10^{-3}(V_{GS} - 5)^2$$

We then plot the input characteristics and the straight line from KVL on the input on the same axis to determine the intersection point.

Voltage-divider biasing for Enhancement-Type MOSFETs

 EXAMPLE 7.11 Determine I_{DQ} , V_{GSQ} , and V_{DS} for the network of Fig. 7.44.



Voltage-divider biasing for Enhancement-Type MOSFETs

EXAMPLE 7.11 Determine I_{DQ} , V_{GSQ} , and V_{DS} for the network of Fig. 7.44.


 


FIG. 7.44

$$\begin{aligned}
 I_{DQ} &\cong 6.7 \text{ mA} \\
 V_{GSQ} &= 12.5 \text{ V} \\
 V_{DS} &= V_{DD} - I_D(R_S + R_D) \\
 &= 40 \text{ V} - (6.7 \text{ mA})(0.82 \text{ k}\Omega + 3.0 \text{ k}\Omega) \\
 &= 40 \text{ V} - 25.6 \text{ V} \\
 &= 14.4 \text{ V}
 \end{aligned}$$

Small Signal Analysis Enhancement-Type MOSFETs

- ❑ E-MOSFET can be either an n-channel (*n*MOS) or *p*MOS device.
- ❑ The ac small-signal equivalent circuit has an open-circuit between gate and drain–source channel.
- ❑ A current source from drain to source having a magnitude dependent V_{GS}
- ❑ Output impedance from drain to source r_d is usually provided on specification sheets as a conductance g_{os} or admittance y_{os} .
- ❑ The device *transconductance* g_m is provided on specification sheets as the forward transfer admittance y_{fs} .

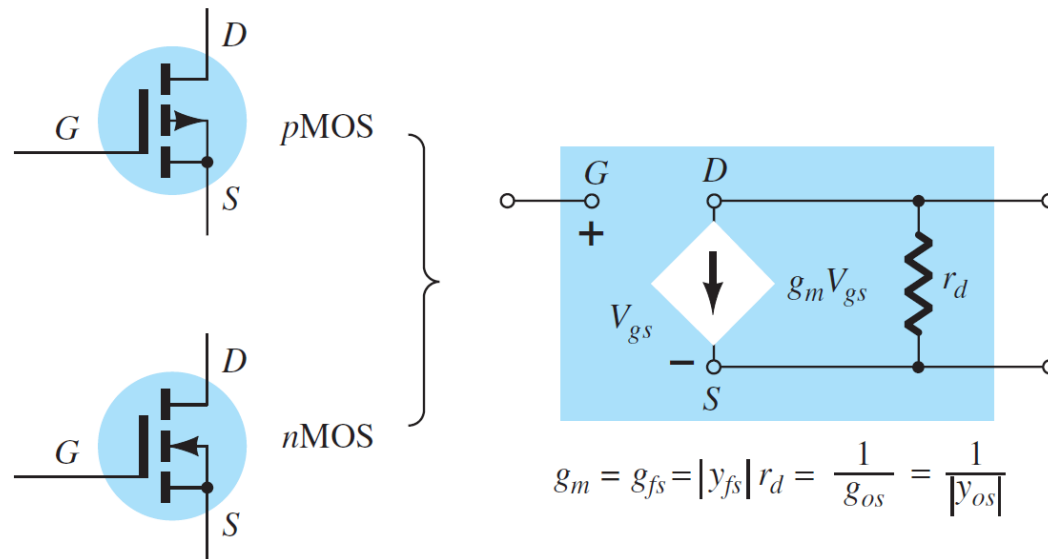

Small Signal Analysis Enhancement-Type MOSFETs

Since g_m is still defined by

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$$

we can take the derivative of the transfer equation to determine g_m as an operating point. That is,

$$\begin{aligned} g_m &= \frac{dI_D}{dV_{GS}} = \frac{d}{dV_{GS}} k(V_{GS} - V_{GS(\text{Th})})^2 = k \frac{d}{dV_{GS}} (V_{GS} - V_{GS(\text{Th})})^2 \\ &= 2k(V_{GS} - V_{GS(\text{Th})}) \frac{d}{dV_{GS}} (V_{GS} - V_{GS(\text{Th})}) = 2k(V_{GS} - V_{GS(\text{Th})})(1 - 0) \end{aligned}$$

and


$$g_m = 2k(V_{GS_Q} - V_{GS(\text{Th})}) \quad (8.45)$$

Small Signal Analysis Enhancement-Type MOSFETs


- ❑ In every other respect, the ac analysis is the same as that employed for JFETs or D-MOSFETs.
- ❑ Be aware, however, that the characteristics of an E-MOSFET are such that the biasing arrangements are somewhat limited.

Small Signal Analysis Enhancement-Type MOSFETs

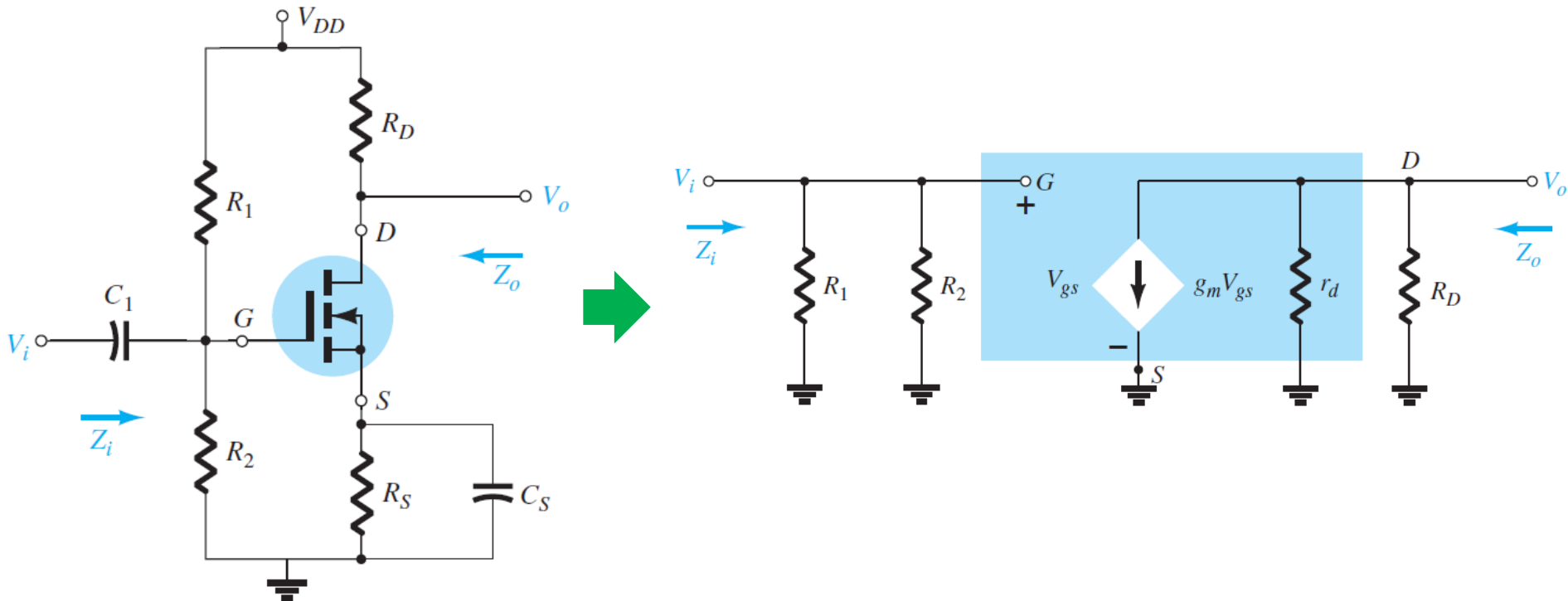- Just as with BJTs you substitute the FET with the small-signal model and short out all capacitors and DC voltage sources.



 Small Signal Analysis Enhancement-Type MOSFETs



Z_i

$$Z_i = R_1 \parallel R_2$$

Z_o

$$Z_o = r_d \parallel R_D$$

For $r_d \geq 10R_D$,

$$Z_o \cong R_D \quad r_d \geq 10R_D$$

and if $r_d \geq 10R_D$,

A_v

$$A_v = \frac{V_o}{V_i} = -g_m(r_d \parallel R_D)$$

$$A_v = \frac{V_o}{V_i} \cong -g_m R_D$$

End of Lecture 7

Thank you for your attention!