

---

# EEE 3571 Electronic Engineering I

---

## Lecture 9: Operational Amplifiers- Non-Inverting Ckts



---

# References


Our main reference text books in this course are

- [1] Neil S., [Electronics: A Systems Approach](#), 4th edition, 2009, Pearson Education Limited, ISBN 978-0-273-71918-2.
- [2] Boylestad R. L., Nashelsky L., [Electronic Devices and Circuit Theory](#), 11<sup>th</sup> Ed, 2013, Prentice-Hall, ISBN 978-0-13-262226-4.
- [3] Smith R. J., Dorf R. C., [Circuits Devices and Systems](#), 5<sup>th</sup> Ed., 2004, John Wiley, ISBN ISBN 9971-51-172-X.

However, feel free to use pretty much any additional text which you might find relevant to our course.

## 9.3 Noninverting Circuit Applications

- In a noninverting circuit, shown in Fig. 1, the input signal is applied to the noninverting + terminal, and a fraction of the output signal is fed back to the inverting – terminal.
- Here  $R_1$  and  $R_F$  constitute a **voltage divider** across the output voltage. For an ideal op amp with  $v_i = 0$ ,

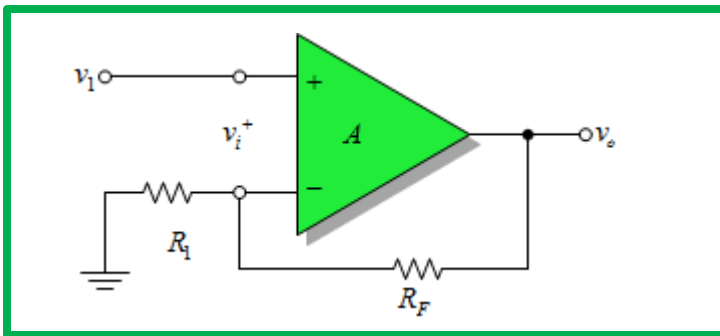

**Fig. 1:** The noninverting amplifier circuit.

$$v_1 - \frac{R_1}{R_1 + R_F} v_o = v_i = 0 \quad [1]$$

Thus, 
$$A_F = \frac{v_o}{v_i} = \frac{R_1 + R_F}{R_1} \quad [2]$$

- This basic noninverting amplifier has two distinctive features.
- First, output signals are in phase with those at the input. Second, the input resistance is very high, approaching infinity in practical terms, and the output resistance is very low.

---

# Noninverting Circuit Applications

- ❑ This implies that noninverting amplifiers do not “load” their sources and, in turn, they are not affected by their loads.


# Voltage Follower

- A useful special case of the noninverting circuit is shown in Fig. 2. Here  $R_F = 0$  and  $R_1 = \infty$  (open circuit). From Eq. [3], the circuit gain is now

$$A_F = \frac{v_o}{v_i} \cong \frac{R_1 + R_F}{R_1} = 1 \quad [3]$$

- The output voltage is just equal to the input voltage and this is the **voltage follower**.

- It is known as a voltage follower because the potential at the  $v_o$  terminal “follows” the potential at the  $v_i$  terminal.

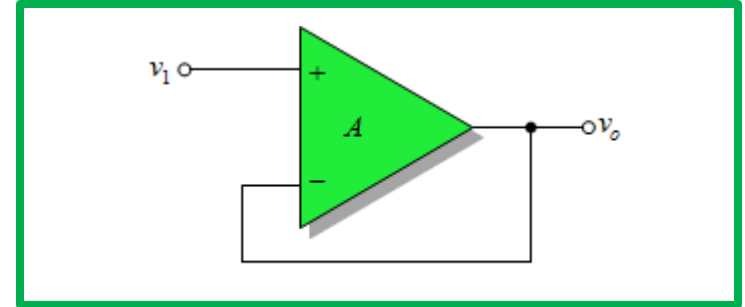

**Fig. 2:** The voltage-follower circuit.

# [Example 1] Noninverting Circuit Applications Cont'd

- Clearly, the circuit in question is a voltage follower with unity gain. With feedback, the input resistance is

$$R_{iF} \cong \frac{v_s}{i_i} \cong \frac{10}{1.01 \times 10^{-9}} \cong 10^{10} \Omega$$

a very high value.

## Unity-Gain Buffer

- Example 1 demonstrates that the gain of a voltage follower is almost exactly 1. Its usefulness lies in its ability to **isolate a high-resistance source** from a **low-resistance load**. To achieve this, the isolating network ought to have a very high input resistance and a very low output resistance.
- In general, such a network is known as a **buffer**. We cannot use the ideal op amp model to derive the general input and output characteristics of such a **unity-gain buffer** since they depend on the non-ideal properties of the op amp.

---


# Noninverting Circuit Applications

## Voltage Regulator

- ❑ The simple **Zener diode** voltage regulator is meant to alleviate the effects of supply voltage fluctuation  $V_1$  and load current variation  $I_L$  on the load voltage  $V_L$ .
- ❑ By using a high-gain amplifier and negative feedback, we can obtain much better regulation.
- ❑ In a **practical power supply**, a transformer provides an ac voltage at the proper level, a **diode rectifier** provides unidirectional current, and a **capacitor filter** develops an unregulated dc voltage. Thus, a **regulator** is added to **alleviate** voltage fluctuations.

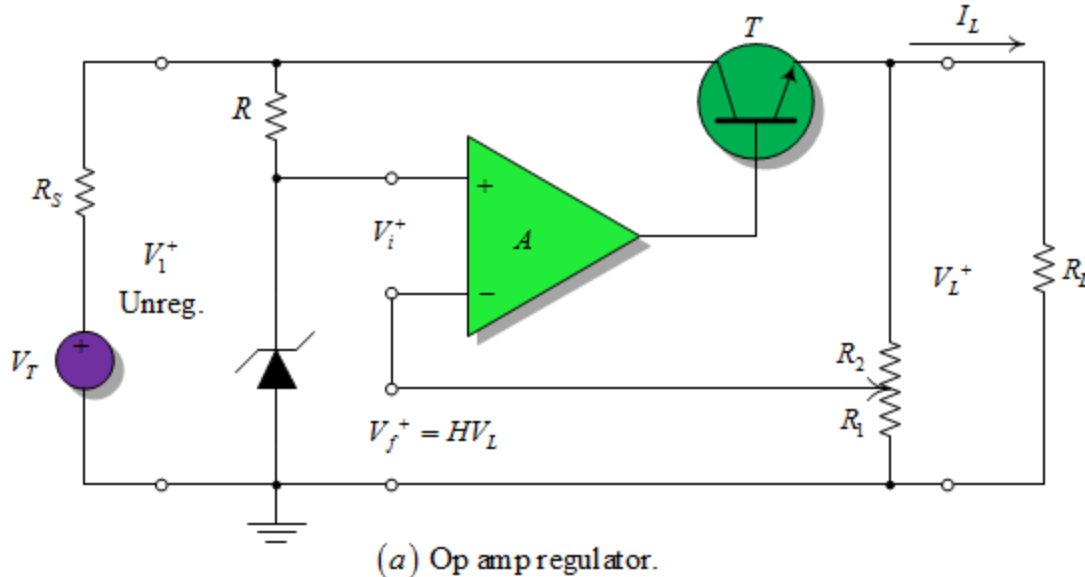
# Voltage Regulator

- In Fig. 6a, transistor  $T$  acts as a variable voltage dropping element, in series, with the load resistance  $R_L$  so that  $V_{CE} = V_1 - V_L$ .
- The op-amp such as 741 is used as a sensitive control of the pass element  $T$ . The Zener diode provides a constant reference voltage  $V_Z = V_p$ .



# Noninverting Circuit Applications

- The variable voltage divider  $R_1$ - $R_2$  takes a fraction  $H = R_1 / (R_1 + R_2)$  of the load voltage  $V_L$  and feeds it back to the inverting terminal so that  $v_n = V_f = HV_L$ .

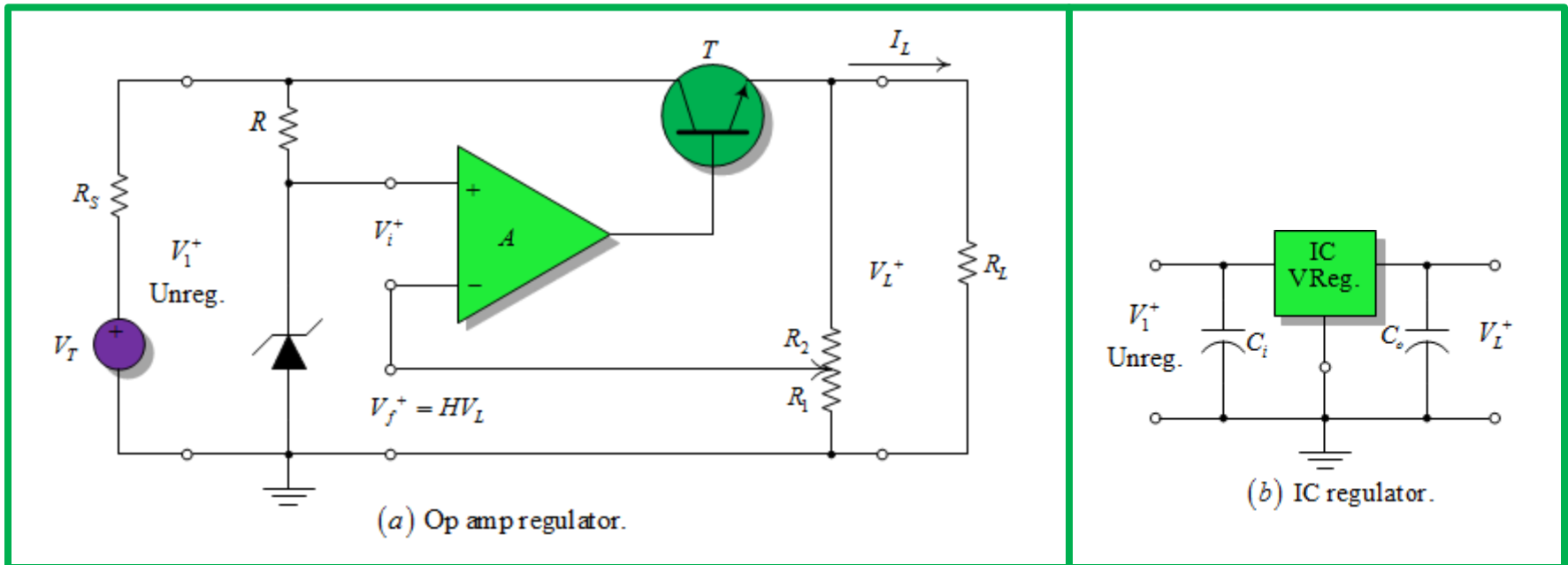

**Fig. 6:** Voltage regulators with feedback.

# Noninverting Circuit Applications

- ❑ In effect, we compare  $V_f$  to the reference voltage  $V_Z$  ; any difference is amplified and used to control the base current to the transistor  $T$ .
- ❑ If for any reason the load voltage tends to drop,  $V_f$  decreases slightly,  $V_i = v_p - v_n$  increases significantly, and the base current to  $T$  increases, increasing emitter current and stabilizing  $V_L$  .
- ❑ The pass transistor must be able to dissipate the power  $P_D = V_{CE}I_L$  ; an adequate “heat sink” is required.
- ❑ The variation of  $V_{BE}$  and  $V_Z$  with temperature is a principal limitation on the voltage stability of the ckt in Fig. 6a. Furthermore, the ckt provides no high-current protection; as a short ckt may destroy  $T$ .
- ❑ To alleviate these difficulties, the sophisticated circuitry in IC form is used, see Fig. 6b. Capacitor  $C_i$  and  $C_o$  improve the operation by reducing the effect of transformer inductance at the input and minimizing the effect of sudden changes in load at the output.

---

## **End of Lecture 2**

**Thank you for your attention!**