

EEE 3571 ELECTRONIC ENGINEERING I
TERM 1 TEST [SOLUTIONS] – 2016/2017 ACADEMIC YEAR – MARCH 30, 2017

[QUESTION 1]

(a)

(i) Determine the thermal voltage for a diode at a temperature of $T = 100^\circ\text{C}$ (boiling point of water). **[4 Marks]**

(ii) For the same diode of part (i), find the diode current if $I_s = 5\mu\text{A}$, $n = 2$ (low value of V_D), and the applied bias voltage is 0.5V . **[4 Marks]**

[SOLUTION]:

(i) To start with we convert the given temperature to absolute value in kelvins, i.e.,

$$T_K = 273 + T(^{\circ}\text{C}); T_K = 273 + 100 = 273\text{K};$$

Thus, thermal voltage is, $V_T = \frac{kT_K}{q} = \frac{(1.38 \times 10^{-23} \text{ J/K})(273\text{K})}{1.602 \times 10^{-19} \text{ C}} = 0.03213\text{V};$

$$\therefore V_T = \mathbf{32.13\text{mV}}.$$

[4 Marks]

(ii) The diode current for the aforesaid diode given, $I_s = 5\mu\text{A}$, $n = 2$, and the applied bias voltage is $V_D = 0.5\text{V}$; is determined using Shockley's eq., i.e.,

$$I_D = I_s (e^{V_D/nV_T} - 1) = (5 \times 10^{-6} \text{ A}) (e^{0.5/2(0.03213)} - 1) = 0.011967\text{A}; I_D = \mathbf{11.967\text{mA}}.$$

[4 Marks]

(b) Given a diode current of 6mA , $V_T = 26\text{mV}$, $n = 1$, and $I_s = 1\text{nA}$, find the applied voltage V_D . **[4 Marks]**

[SOLUTION]:

Given $I_D = 6\text{mA}$, $V_T = 26\text{mV}$, $n = 1$, and $I_s = 1\text{nA}$, V_D is found as follows:

$$I_D = I_s (e^{V_D/nV_T} - 1); \Rightarrow e^{V_D/nV_T} = \left(\frac{I_D}{I_s} \right) + 1, \text{ thus,}$$

$$V_D = nV_T \ln \left[\left(\frac{I_D}{I_s} \right) + 1 \right] = (0.026) \ln \left[\left(\frac{6 \times 10^{-3}}{10^{-9}} \right) + 1 \right] = 0.405789; V_D = \mathbf{405.789\text{mV}}.$$

[4 Marks]

(c) The network shown in Figure Q1 is a fixed input voltage V_i and variable load R_L

(i) Determine V_L , I_L , I_Z , and I_R for the network of Figure Q1(a) if $R_L = 180\Omega$. **[7 Marks]**

(ii) Determine the value of R_L that will establish maximum power conditions for the Zener diode. **[3 Marks]**

(iii) Determine the minimum value of R_L to ensure that the Zener diode is in the "on" state. **[3 Marks]**

[3 Marks]


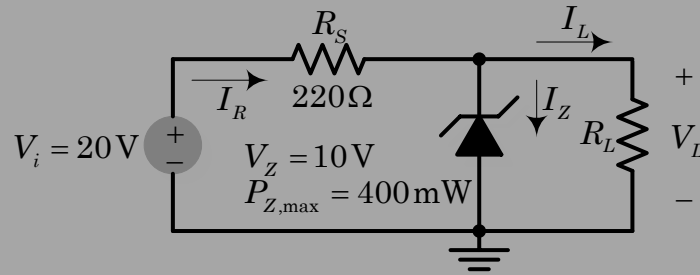


Figure Q1.

[Total 25 Marks]

[SOLUTION]:

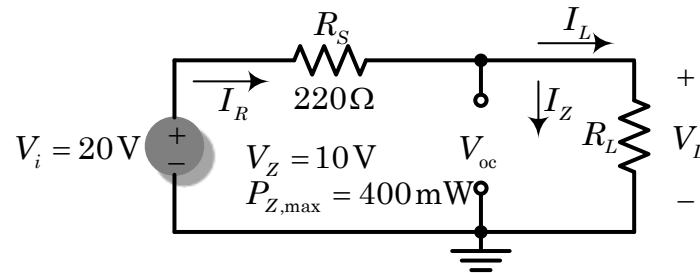- (i) **Step 1:** Remove Zener diode and determine open circuit voltage with $R_L = 180\ \Omega$, i.e.,



[1 Mark]

$$V_{oc} = V_L = \frac{R_L}{R_s + R_L} V_i = \frac{180}{180 + 220} (20\text{ V}) = 9\text{ V}, \text{ Thus, } V_L = 9\text{ V}.$$

[2 Marks]

Notice that $V_L < V_Z = 10\text{ V}$, thus the diode is OFF the equivalent circuit is an open circuit.

$$\text{It follows that, } I_L = \frac{V_L}{R_L} = \frac{9\text{ V}}{180\ \Omega} = 0.05; \quad I_L = 50\text{ mA}.$$

[2 Mark]


$$\text{Vividly, } I_Z = 0\text{ V}.$$

[1 Mark]

$$\text{Finally, } I_R = I_L + I_Z = 50\text{ mA}.$$

[1 Mark]

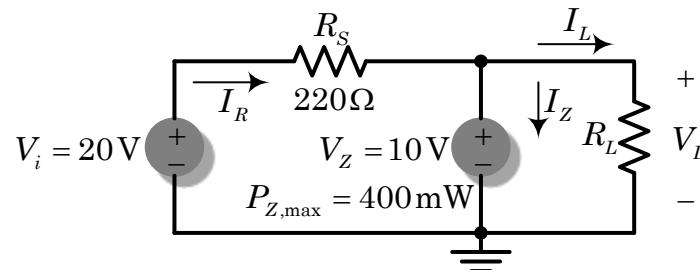- (ii) For maximum power condition the diode should be ON and its equivalent circuit is as shown,



$$P_{Z,max} = I_{Z,max} V_Z, \text{ thus, } I_{Z,max} = \frac{P_{Z,max}}{V_Z} = \frac{400\text{ mW}}{10\text{ V}} = 40\text{ mA}; \text{ it follows that,}$$

$$I_R = \frac{V_i - V_Z}{R_s} = \frac{20\text{ V} - 10\text{ V}}{220\ \Omega} = 0.0454545\text{ A}; \quad I_R = 45.4545\text{ mA}, \text{ and } I_{L,min} = I_R - I_{Z,max};$$

$$\text{Thus, } R_{L,max} = \frac{V_L}{I_{L,min}} = \frac{10\text{ V}}{(45.4545 - 40)\text{ mA}} = 1833.33\ \Omega, \quad R_{L,max} = 1.833\text{ k}\Omega \quad [3\text{ Marks}]$$

- (iii) For the diode to be ON, $R_{L,min}$ ought to be, $R_{L,min} = \frac{R_s V_Z}{V_i - V_Z} = \frac{(220\ \Omega)(10\text{ V})}{20\text{ V} - 10\text{ V}} = 220\ \Omega;$

$$R_{L,min} = 220\ \Omega.$$

[3 Marks]

[Total 25 Marks]

[QUESTION 2]**(a)**

(i) Use your knowledge of differential calculus to find the derivative dI_D/dV_D of the diode characteristics function $I_D = I_s(e^{V_D/nV_T} - 1)$. **[5 Marks]**

(ii) Hence, by assuming $I_D \gg I_s$ in the vertical-slope section of the diode characteristics, show that the dynamic resistance (ac resistance) is given by $r_d = dV_D/dI_D = nV_T/I_D$. **[5 Marks]**

[SOLUTION]:

(i) The derivative of the diode characteristic eq. is found using the calculus as

$$\frac{dI_D}{dV_D} = \frac{d}{dV_D} I_s (e^{V_D/nV_T} - 1) = \frac{I_s e^{V_D/nV_T}}{nV_T}; \text{ but } I_s e^{V_D/nV_T} = I_D + I_s;$$

This implies that, $\frac{dI_D}{dV_D} = \frac{I_s e^{V_D/nV_T}}{nV_T} = \frac{I_D + I_s}{nV_T}$. **[5 Marks]**

(ii) Assuming $I_D \gg I_s$, we have $I_D + I_s \cong I_D$; i.e., $I_s e^{V_D/nV_T} \cong I_D$; thus,

$$\frac{dI_D}{dV_D} = \frac{I_D}{nV_T}; \text{ inverting this results yields}$$

$$r_d = \frac{dV_D}{dI_D} = \frac{nV_T}{I_D}. \text{ Hence shown.} \quad \mathbf{[5 Marks]}$$

(b) For the emitter follower network of Figure Q2,

(i) Find I_B , I_C , and I_E . **[6 Marks]**

(ii) Find V_B , V_C , and V_E . **[6 Marks]**

(iii) Calculate V_{BC} and V_{CE} . **[3 Marks]**


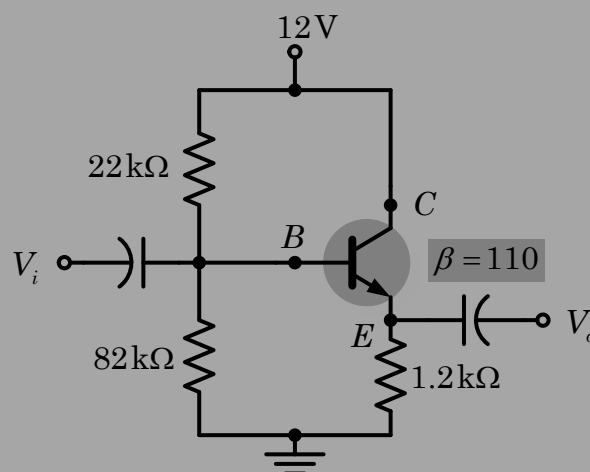


Figure Q2.

[Total 25 Marks]

[SOLUTION]:

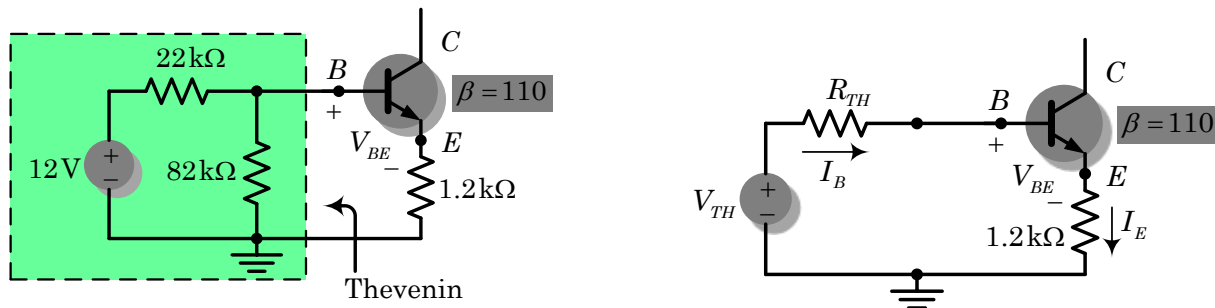(i) To do dc analysis, the ac sources are switched OFF. Thus, the input circuit becomes



Where, $R_{TH} = 22\text{k}\Omega \parallel 82\text{k}\Omega = 17.34615\text{k}\Omega$, $V_{TH} = \frac{82\text{k}\Omega}{82\text{k}\Omega + 22\text{k}\Omega}(12\text{V}) = 9.461538\text{V}$;

Applying KVL to the resultant input circuit yields, $V_{TH} - I_B R_{TH} - V_{BE} - I_E R_E = 0$;


But, $I_E = (\beta + 1)I_B$; thus, $V_{TH} - V_{BE} - (R_{TH} + (\beta + 1)R_E)I_B = 0$; from which we get

$$I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (\beta + 1)R_E} = \frac{9.461538\text{V} - 0.7\text{V}}{17.346154\text{k}\Omega + (111)(1.2\text{k}\Omega)} = 5.81984 \times 10^{-5};$$

$$I_B = \mathbf{58.1984\ \mu\text{A}}$$

[4 Marks]

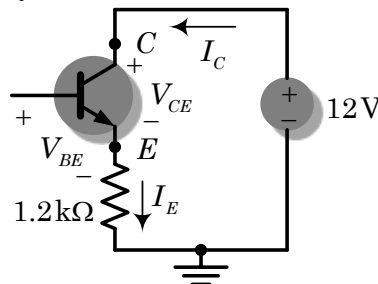Applying KVL to the output circuit yields,



$I_E R_E + V_{CE} - 12 = 0$; since $I_E \cong I_C$; we have

$$I_E = (\beta + 1)I_B = 111(58.1984 \times 10^{-6}\text{A}) = 0.006460\text{A}; \quad I_C = \beta I_B = 0.0064018\text{A};$$

$$I_E = \mathbf{6.460\text{mA}}; \quad I_C = \mathbf{6.4018\text{mA}}.$$

[2 Marks]

(ii) To determine V_B , we use

$$V_B = V_{TH} - I_B R_{TH} = 9.461538\text{V} - (5.81984 \times 10^{-5}\text{A})(17.34615 \times 10^3\Omega) = 8.4520\text{V};$$

$$V_B = \mathbf{8.4520\text{V}}.$$

[2 Marks]

Vividly, $V_C = \mathbf{12\text{V}}$.

[2 Marks]

Furthermore, $V_E = V_B - V_{BE} = 8.4520\text{V} - 0.7\text{V} = 7.7520\text{V}$; $V_E = \mathbf{7.7520\text{V}}$.

[2 Marks]

Alternatively, $V_E = I_E R_E = (0.006460\text{A})(1200\Omega) = \mathbf{7.7520\text{V}}$.


(iii) Thus, $V_{BC} = V_B - V_C = 8.4520\text{V} - 12\text{V} = \mathbf{-3.5480\text{V}}$; which confirms the base collector junction being reverse biased.

[1.5 Marks]


Finally, $V_{CE} = V_C - V_E = 12\text{V} - 7.7520\text{V} = \mathbf{4.2480\text{V}}$.

[1.5 Marks]

[Total 25 Marks]

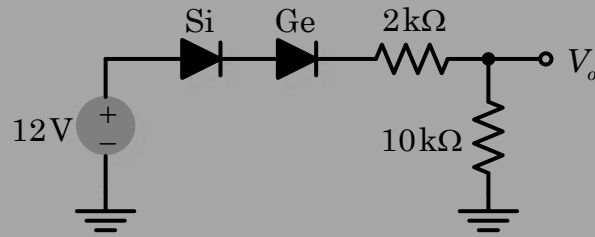[QUESTION 3](a) Determine the level of voltage V_o for network of Figure Q3(a).**[5 Marks]****Figure Q3(a).****[SOLUTION]:**


By exploiting the constant diode voltage drop model for both diodes the equivalent circuit is;

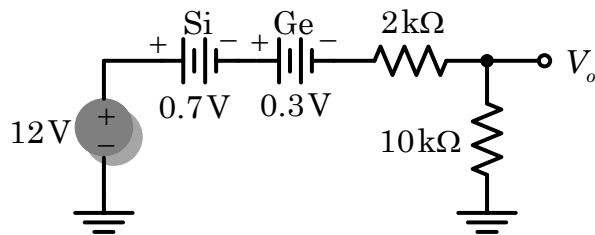**[2 Marks]**


Using potential divider we have,

$$V_o = \frac{10\text{k}\Omega}{2\text{k}\Omega + 10\text{k}\Omega} (12\text{V} - 0.7\text{V} - 0.3\text{V}) = \frac{5}{6} (11\text{V}) = 9.16667\text{V}; \quad V_o = \mathbf{9.1667\text{V}}. \quad \mathbf{[3\text{ Marks}]}$$

(b) For the network of Figure Q3(b):

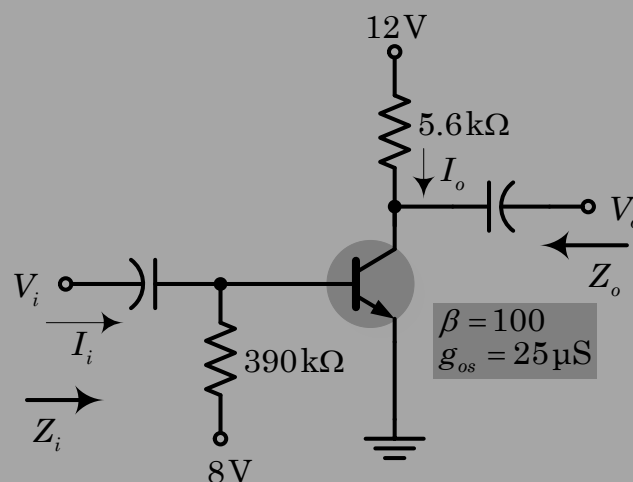(i) Calculate I_B , I_C , and r_e .**[6 Marks]**(ii) Determine Z_i and Z_o .**[8 Marks]**(iii) Calculate A_v .**[4 Marks]**(iv) Determine the effect of $r_o = 30\text{ k}\Omega$ on A_v .**[2 Marks]****Figure Q3(b).****[Total 25 Marks]****[SOLUTION]:**

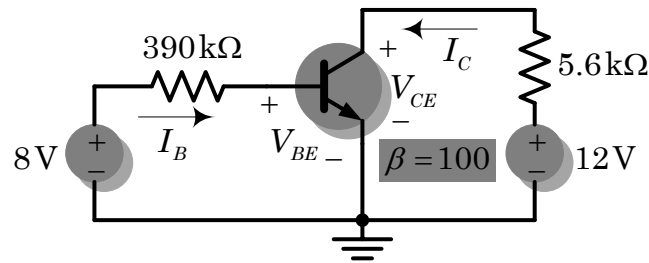(i) First we perform dc analysis by switching OFF ac voltage sources, i.e.,



[1 Mark]

Clearly, $V_B = V_{BE} = 0.7 \text{ V}$ since the emitter is connected to the ground.

$$\text{Thus, } I_B = \frac{8 \text{ V} - 0.7 \text{ V}}{390 \text{ k}\Omega} = 1.871795 \times 10^{-5}; \quad I_B = \mathbf{18.718 \mu\text{A}}.$$

[2 Marks]

Furthermore, $I_C \cong I_E = (\beta + 1)I_B = 101(18.1795 \times 10^{-6} \text{ A}) = 0.00189051 \text{ A};$

$$I_C \cong I_E = \mathbf{1.8905 \text{ mA}}.$$


[1 Mark]

Therefore,

$$r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{1.8905 \text{ mA}} = 13.752975 \Omega; \quad r_e = \mathbf{13.753 \Omega}$$

[2 Marks]

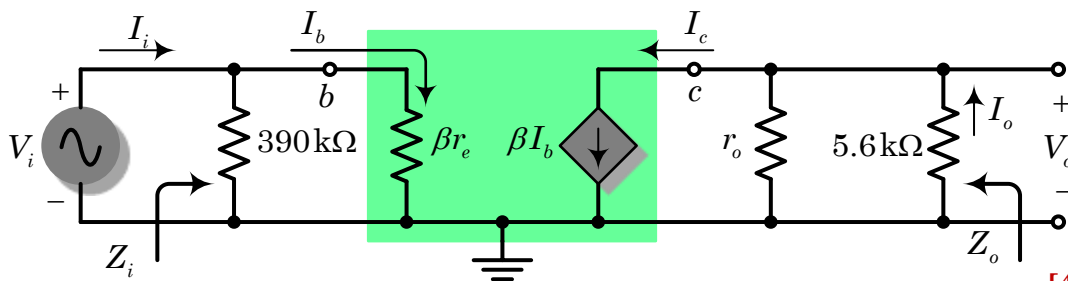(ii) We now conduct ac analysis in order to determine Z_i and Z_o , that is, substituting the r_e model yields



[4 Marks]

From the ac equivalent circuit above,

$$Z_i = 390 \text{ k}\Omega \parallel \beta r_e = 390 \text{ k}\Omega \parallel (100)(13.753 \Omega) = 390 \text{ k}\Omega \parallel 1.3753 \text{ k}\Omega = 1.3705 \text{ k}\Omega;$$

$$Z_i = \mathbf{1.3705 \text{ k}\Omega}.$$

[2 Marks]

Clearly, if $V_i = 0$, $I_i = I_b = 0$; $r_o = 1/g_{os} = 1/25 \mu\text{S} = 40 \text{ k}\Omega$;

$$Z_o = 5.6 \text{ k}\Omega \parallel 40 \text{ k}\Omega = \mathbf{4.9123 \text{ k}\Omega}.$$

[2 Marks]

(iii) To determine the voltage gain A_v , we start by formulating equations, i.e.,

$$I_b = \frac{V_i}{\beta r_e}; \quad \text{also } V_o = -\beta I_b (r_o \parallel 5.6 \text{ k}\Omega), \quad \text{thus, } V_o = -\beta \left(\frac{V_i}{\beta r_e} \right) (r_o \parallel 5.6 \text{ k}\Omega);$$

Therefore, with $r_o = 40 \text{ k}\Omega$, $Z_o = 5.6 \text{ k}\Omega \parallel 40 \text{ k}\Omega = 4.912281 \text{ k}\Omega$, so that ,

$$A_v = \frac{V_o}{V_i} = -\frac{5.6 \text{ k}\Omega \parallel 40 \text{ k}\Omega}{r_e} = -\frac{4.912281 \text{ k}\Omega}{13.752975 \Omega} = \mathbf{-357.18}.$$

[4 Marks]

(iv) With $r_o = 30 \text{ k}\Omega$, $Z_o = 5.6 \text{ k}\Omega \parallel 30 \text{ k}\Omega = 4.7191 \text{ k}\Omega$, so that ,

$$A_v = \frac{V_o}{V_i} = -\frac{5.6 \text{ k}\Omega \parallel 30 \text{ k}\Omega}{r_e} = -\frac{4.7191 \text{ k}\Omega}{13.752975 \Omega} = \mathbf{-343.13}.$$

[2 Marks]

Notice that $r_o = 30 \text{ k}\Omega$ causes the voltage gain A_v to reduce slightly.

[Total 25 Marks]

[QUESTION 4]

(a) Determine V_o and I_D for the network of Figure Q4(a).

[7 Marks]


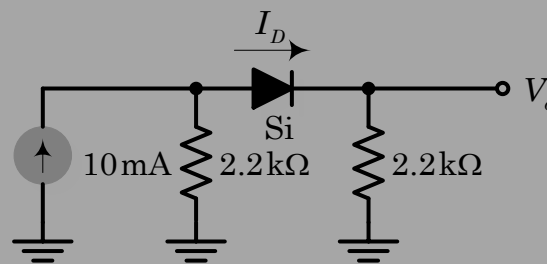


Figure Q4(a).

[SOLUTION]:

The circuit is redrawn with the Thevenin equivalent circuit replacing the Norton current source and resistance. Also the diode is replaced with a battery. That is,
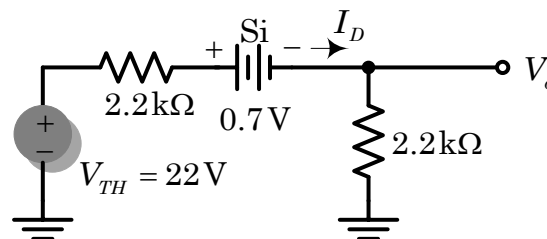
$$V_{TH} = I_N R_N = (10\text{mA})(2.2\text{k}\Omega) = 22\text{V}, \text{ and } R_{TH} = R_N = 2.2\text{k}\Omega,$$



[2 Marks]

Thus, by potential divider, $V_o = \left(\frac{2.2\text{k}\Omega}{2.2\text{k}\Omega + 2.2\text{k}\Omega} \right) (22\text{V} - 0.7\text{V}) = 10.65\text{V}$.

[3 Marks]

It follows that, $I_D = \frac{10.65\text{V}}{2.2\text{k}\Omega} = 4.8409\text{mA}$.

[2 Marks]

(b) For the cascaded system of Figure Q4(b), determine:

(i) The loaded voltage gain of each stage. [4 Marks]

(ii) The total gain of the system, $A_{v,L}$ and $A_{v,S}$. [4 Marks]

(iii) The loaded current gain of each stage. [4 Marks]

(iv) The total current gain of the system. [2 Marks]

(v) How Z_i is affected by the second stage and R_L . [1 Mark]

(vi) How Z_o is affected by the first stage and R_S . [1 Mark]

(vii) The phase relationship between V_o and V_i . [2 Marks]

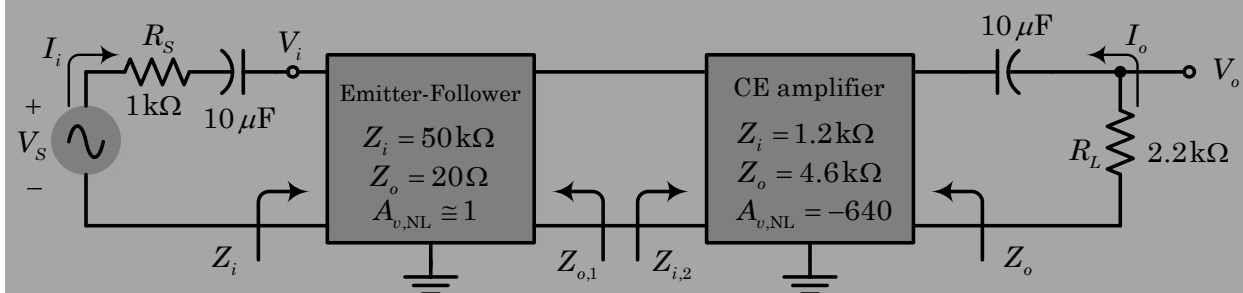


Figure Q4(b).

[Total 25 Marks]

[SOLUTION]:

(i) The loaded gain of each stage is obtained as follows,

$$\text{For the Emitter follower: } V_{o,1} = \frac{Z_{i,2}}{Z_{i,2} + Z_{o,1}} A_{v,NL} V_{i,1} = \left(\frac{1.2\text{k}\Omega}{1.2\text{k}\Omega + 0.02\text{k}\Omega} \right) (1) V_{i,1} = 0.9836 V_{i,1};$$

$$\text{Thus, } A_{v_{1,L}} = \frac{V_{o,1}}{V_{i,1}} = \mathbf{0.9836} . \quad [2 \text{ Marks}]$$

$$\text{Furthermore, } V_{o,2} = \frac{R_L}{R_L + Z_{o,2}} A_{v,NL} V_{i,2} = \left(\frac{2.2\text{k}\Omega}{2.2\text{k}\Omega + 4.6\text{k}\Omega} \right) (-640) V_{i,1} = -207.05882 V_{i,1}$$

$$A_{v_{2,L}} = \frac{V_{o,2}}{V_{i,2}} = \mathbf{-207.0588} . \quad [2 \text{ Marks}]$$

(ii) The total gain of the system is,

$$A_{v,T} = \left(\frac{V_{o,1}}{V_{i,1}} \right) \left(\frac{V_{o,2}}{V_{i,2}} \right) = (0.9836) (-207.0588) = \mathbf{-203.6630} . \quad [2 \text{ Marks}]$$

The total gain of the system with source resistance included,

$$V_{o,2} = \frac{Z_{i,1}}{Z_{i,1} + R_S} A_{v,T} V_S; \text{ so that,}$$

$$A_{v,S} = \frac{V_{o,2}}{V_S} = \frac{Z_{i,1}}{Z_{i,1} + R_S} A_{v,T} = \left(\frac{50\text{k}\Omega}{50\text{k}\Omega + 1\text{k}\Omega} \right) (-203.6630) = -199.6630;$$

$$A_{v,s} = \frac{V_{o,2}}{V_S} = \mathbf{-199.6630} . \quad [2 \text{ Marks}]$$

(iii) It follows that the loaded current gain is,

For the emitter-follower,

$$A_{i_{1,L}} = \frac{I_{o,1}}{I_{i,1}} = -A_{v_{1,L}} \frac{Z_{i,1}}{Z_{i,2}} = -(0.9836) \left(\frac{50\text{k}\Omega}{1.2\text{k}\Omega} \right) = \mathbf{-40.9833} . \quad [2 \text{ Marks}]$$

$$A_{i_{2,L}} = \frac{I_{o,2}}{I_{i,2}} = A_{v_{2,L}} \frac{Z_{i,2}}{R_L} = (-207.05882) \left(\frac{1.2\text{k}\Omega}{2.2\text{k}\Omega} \right) = \mathbf{-112.9412} . \quad [2 \text{ Marks}]$$

(iv) Thus the overall current gain is,

$$A_{i,T} = \frac{I_{o,2}}{I_{i,1}} = -A_{v,S} \frac{R_S + Z_{i,1}}{R_L} = -(-199.6630) \left(\frac{1\text{k}\Omega + 50\text{k}\Omega}{2.2\text{k}\Omega} \right) = \mathbf{4628.55} . \quad [2 \text{ Marks}]$$

(v) Z_i is NOT affected by the second stage and R_L . [2 Marks]

(vi) Z_o is NOT affected by the first stage and R_S .

(vii) The output voltage V_o is 180° out of phase from the input voltage V_i . [2 Marks]

[Total 25 Marks]