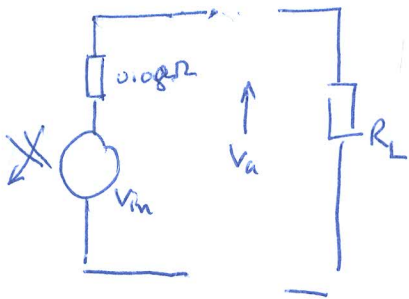


Assignment 8

1. $V_{n.L} = 131V$, $n = 5000 \text{ rpm}$, $NI = 2000A$, $R_a = 0.08 \Omega$, $I_a = 150A$



$$V_a = V_{in} - I_a R_a$$

$$= 131 - 0.08 (150) = \underline{119V} \quad 10$$

$$P_{out} = I_a V_a = 150 \times 119 = \underline{17.85 \text{ kW}} \quad 10$$

$$P_{in} = V_{in} I_a = 131 \times 150 = \underline{19.65 \text{ kW}} \quad 10$$

$$T_{e_{in}} = \frac{1}{2\pi} \frac{19650}{5000/60} = \underline{37.53 \text{ Nm}} \quad 10$$

2. From plot: $V_{oc_{1200rpm}} = 770V$; $V_{oc_{1000rpm}} = \frac{770}{1200} \times 1000 = 640V = V_{in}$

$$I_a = \frac{640}{1 + \frac{5 \times 120}{5 + 120}} = 110.3A \quad 20$$

$$I_s = 110.3 \times \frac{120}{120 + 5} = \underline{106A} \quad 20$$

$$V_s = V_{in} - I_a R_a = 640 - 110.3 \times 1 = \underline{530V} \quad 20$$

