

# EEE 3352

## Electromechanics & Electrical Machines



## Lecture 7: Introduction to power systems

Dr A Zulu © 2021



# 7. Introduction to Power Systems

1. Energy: system viewpoint
2. Transmission system
3. HVAC transmission
4. Three phase power systems
  - 1) balanced star
  - 2) balanced delta
5. Measurement of power in three phase systems



## Objectives:

- at the end of the lecture, students should be able to
  - **explain** the importance of electrical energy in systems
  - **justify** the role electrical power in energy systems
  - **explain** the features of electrical transmission systems
  - **justify** the use of three phase systems
  - **derive** relations of one-phase and three-phase quantities in star and delta configurations
  - **show** effective methods to measure power in three phase systems
  - **apply** appropriate methods to measure power in three phase systems



## 7.1 Energy: System Viewpoint

1. Introduction
2. Types of Energy
3. Uses of energy
4. Sources of Energy
5. Conversion of emergy
6. Storage of Energy
7. Transmission of Energy
8. Role of Electric Power
9. Competitive Uses of Natural Sources



## 7.1.1 Introduction

- Energy is essential for life
- Energy also determines quality of life
- There many **sources** of energy
- There many **uses** of energy
- thus USES (NEEDS) vs SOURCES



## 7.1.2 Types of Energy & Power

- “Capacity to do work”
  - Energy  $\gg$  Power
- **Energy**: term relevant for storage
  - *oil tanker, coal mine, water reservoir, battery, etc*
- **Power**: term relevant for flow of energy
  - *rotating shaft, electric cable, gas pipe-line, etc*



## 7.1.3 Uses of Energy

- Heating / cooling
- Motion
- Lighting
- Electrochemical processing
- ICT



## 7.1.4 Sources of Energy

- Non-renewable

- coal
- oil
- natural gas
- nuclear fuel

Fossil fuels

- Renewable

- solar
- hydro
- wind
- bio-energy
- geothermal
- tidal & ocean

## Characteristics of RE & Non RE Energy

	<b>Renewable</b>	<b>Non Renewable</b>
<b>Location</b>	Natural local environment	Relatively concentrated regions
<b>Availability</b>	A given average <b>power</b>	A given amount of stored <b>energy</b>
<b>Life time of supply</b>	No limit	Coal: 100-1000 years; oil: 10-100 years
<b>Cost</b>	High capital, but low running costs	Moderate to high capital; Moderate running costs



## 7.1.5 Energy Conversion

- “law of conservation of energy”

- conversion processes

- chemical  $\leftrightarrow$  thermal : burning wood / endothermic reaction
- thermal  $\leftrightarrow$  mechanical : ? / ?
- thermal  $\leftrightarrow$  electrical : ? / ?
- potential  $\leftrightarrow$  kinetic : ? / ?
- mechanical  $\leftrightarrow$  electrical : ? / ?
- electrical  $\leftrightarrow$  thermal : ? / ?
- electrical  $\leftrightarrow$  chemical : ? / ?

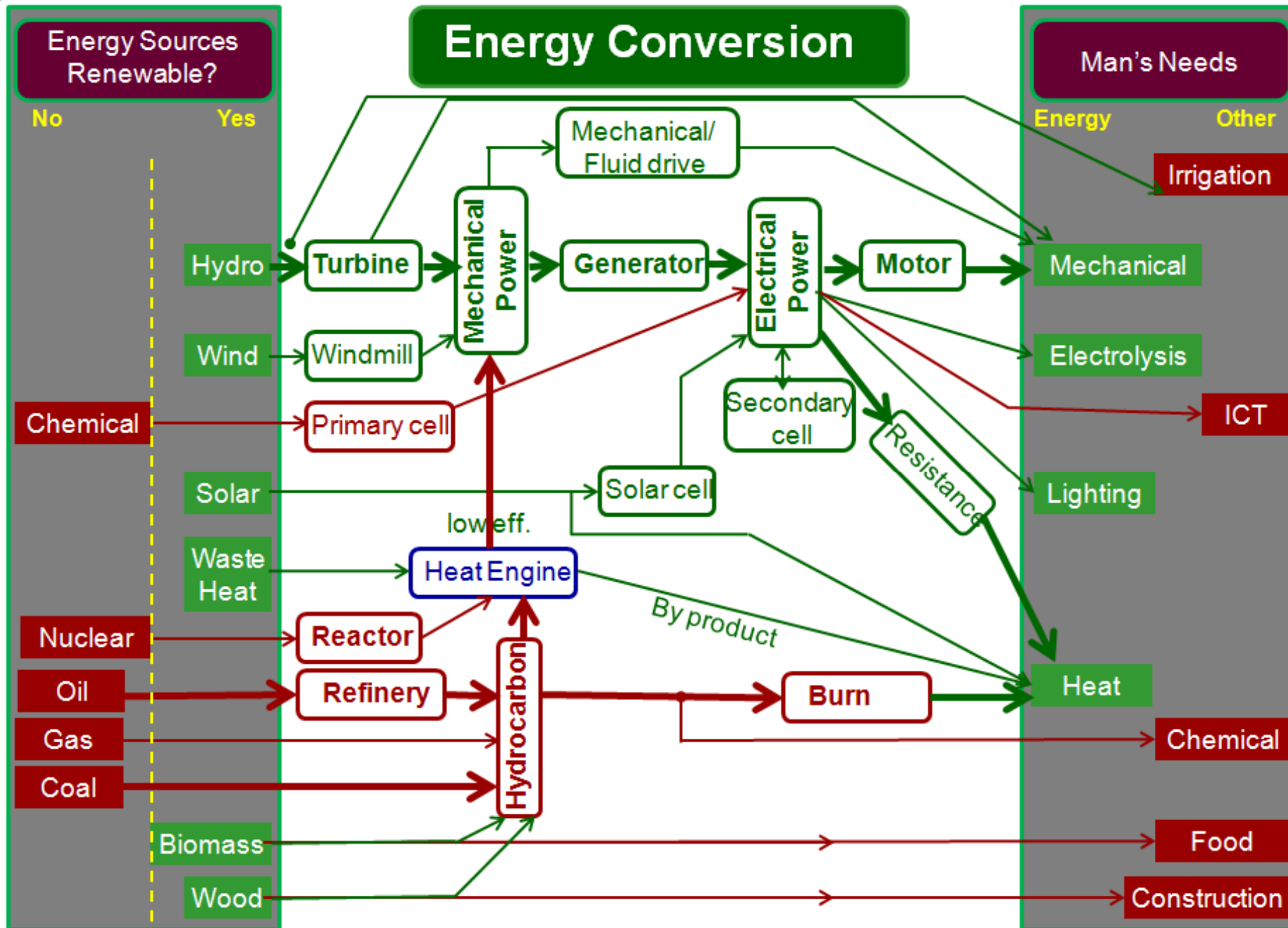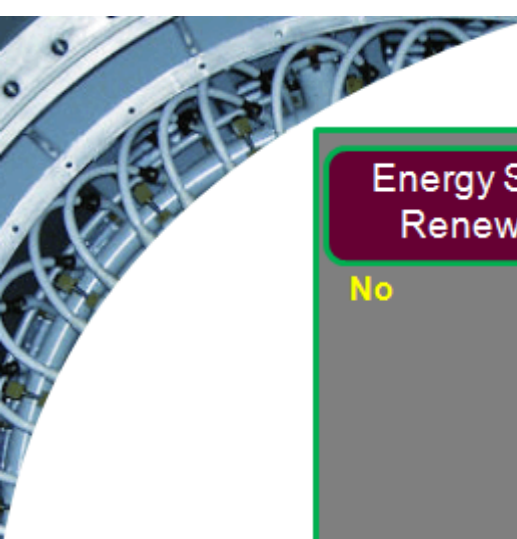- think of an example for each of these conversions





## 7.1.6 Storage of Energy

- **Intermittent Supply**

- solar -charge batteries
- wind -fill up water resv
- river - lake
- petrol engine -flywheel
- dc - capacitor/inductor
- oil tanker
- mechanical spring

- **Intermittent Demand**

- pneumatic drill
- starter motor-battery
- “pumped storage”
- steam pressure in boiler
- capacitors - high spark discharge



## 7.1.7 Transmission of Energy

- Geographical & geological features of the earth determine the **sources** of energy
  - [oil, coal, hydro power, etc]
- Other different features influence where energy is **needed**
  - [in towns, mining, industry, farming]
- Usually **sources** and places of **utilization** are separate
  - so, **transmission** of energy becomes important



## 7.1.8 Transmission of Energy

- **continuous** transmission
- **batch** transmission

# Transmission of Energy

Distance	Continuous	Batch
Long (over 1000 km)	Oil pipeline, gas pipeline, HVAC, HVDC	Oil tanker, coal ships
Medium (1-1000 km)	Oil & gas pipeline, Medium to high voltage	Oil in vehicle, tank, coal in trains, biomass in truck
Short (10m-1km)	Gas pipe, elec(low, high Voltage) conveyor, flues	Biomass in truck, wood
Same building [under 30m]	As in Short	Solid fuel by hand or truck




## 7.1.9 Role of Electrical Power

- Disadvantages

- it does not occur naturally
- not required as end-product (except in electrolysis, communication & computing)
- Cannot be directly stored

- Advantages

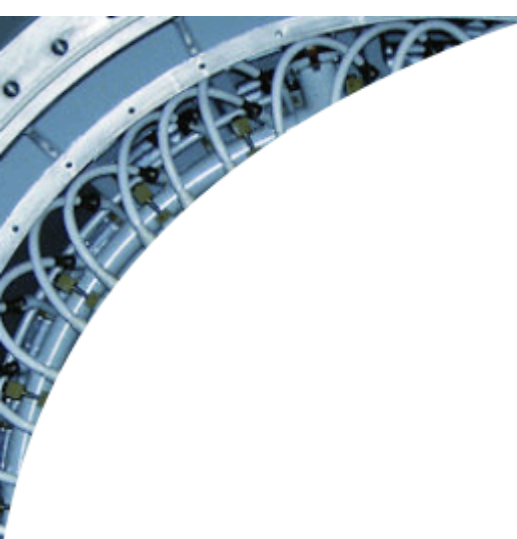- high conversion efficiency
- ease of transmission
- high transmission efficiency
- flexible distribution



## 7.1.9 Role of Electrical Power - A summary


Role	Electrical form	Performance
Use	N	N/A
Source	N	N/A
Conversion	Y	High efficiency
Transmission	Y	High efficiency



## 7.1.10 Competitive Uses of Sources

- Best balance of alternative sources and competitive needs
- Environmental issues
  - extra carbon-dioxide and global warming
  - nuclear waste
  - non-renewable resources


## 7.2 Transmission system

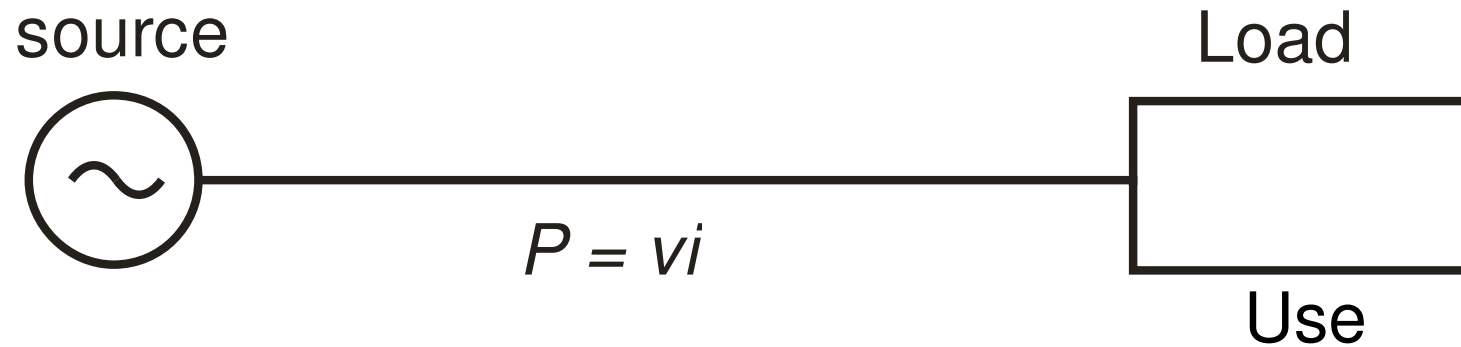

- line losses

$$P_{loss} = 2(i^2 R) = 2 \left( i^2 \frac{\rho l}{A} \right)$$

- for 2 lines – forward and return conductor


- 
- to reduce power losses
    - reduce  $R$  ( limited)
    - reduce  $i$
  - to transmit the same power, reduce  $i$  and increase  $v$
  - hence high voltage (HV) transmission systems



## 7.2.1 HV transmission system

- generation is limited to approx 20 kV, due to insulation requirements
- loads are limited to approx 10 kV due to
  - safety
  - size
  - insulation
- we must change voltage levels to transmit high power
- to change voltage levels, we must use
  - transformer
  - hence ac system

## 7.2.2 High voltage AC system (HVAC)

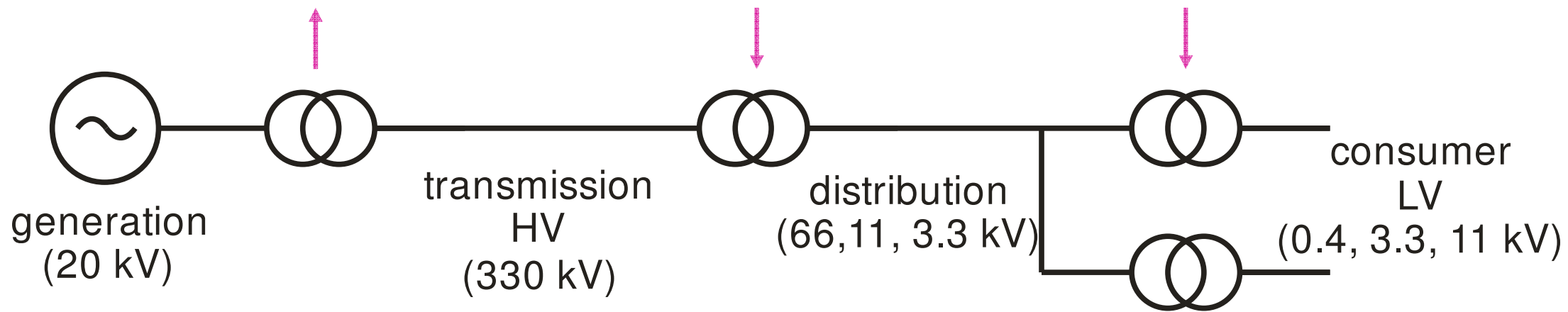



- generation

- up to 25 kV (18 kV)

- transmission

- 110 kV – 1000 kV ( 66, 110, 132, 220, 330, 400, 525, 750 kV)


- distribution


- 3.3 kV – 88 kV ( 3.3, 6.6, 11, 33 kV)

- consumer

- 0.19 -15 kV ( 0.4, 0.55, 3.3, 6.6, 11 kV)

## 7.2.3 High voltage DC system (HVDC)

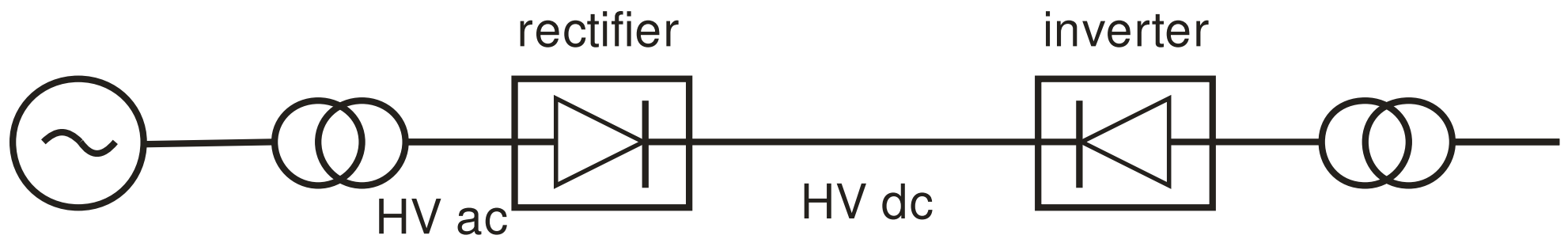

- 
- HVDC is employed where
    - transmission over larger distances (  $> 500$  km)
    - interconnection of systems with different systems
      - (eg 50 Hz to 60 Hz)
    - back-to-back in a substation for power flow control




- Examples

- Gotland – Mainland Sweden (1954) – submarine cable
- Xiangjiaba – Shanghai (2071 km, 6400 MW) - longest
- Inga-Shaba (Congo)
- Cabora-Bossa – RSA

## 7.3 HVAC

### Single phase and 3-phase

Single phase:

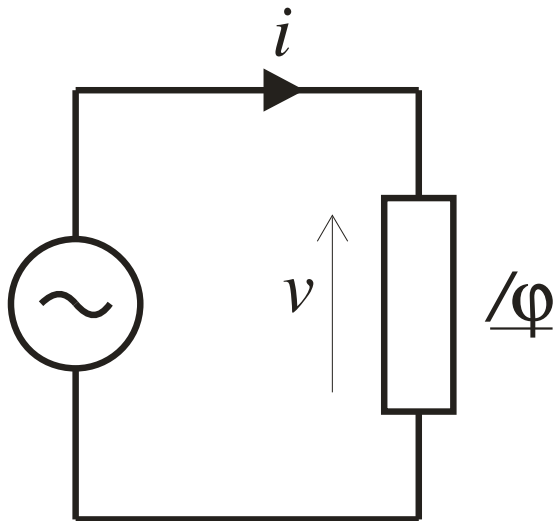

$$v = V_m \sin \omega t$$

$$i = I_m \sin(\omega t - \phi)$$

$$P = V_m I_m \sin \omega t \cdot \sin(\omega t - \phi)$$

$$P = V_m I_m \frac{1}{2} [\cos \phi - \cos(2\omega t - \phi)]$$


$$P = VI \cos \phi - VI \cos(2\omega t - \phi)$$



constant




varying at 2f

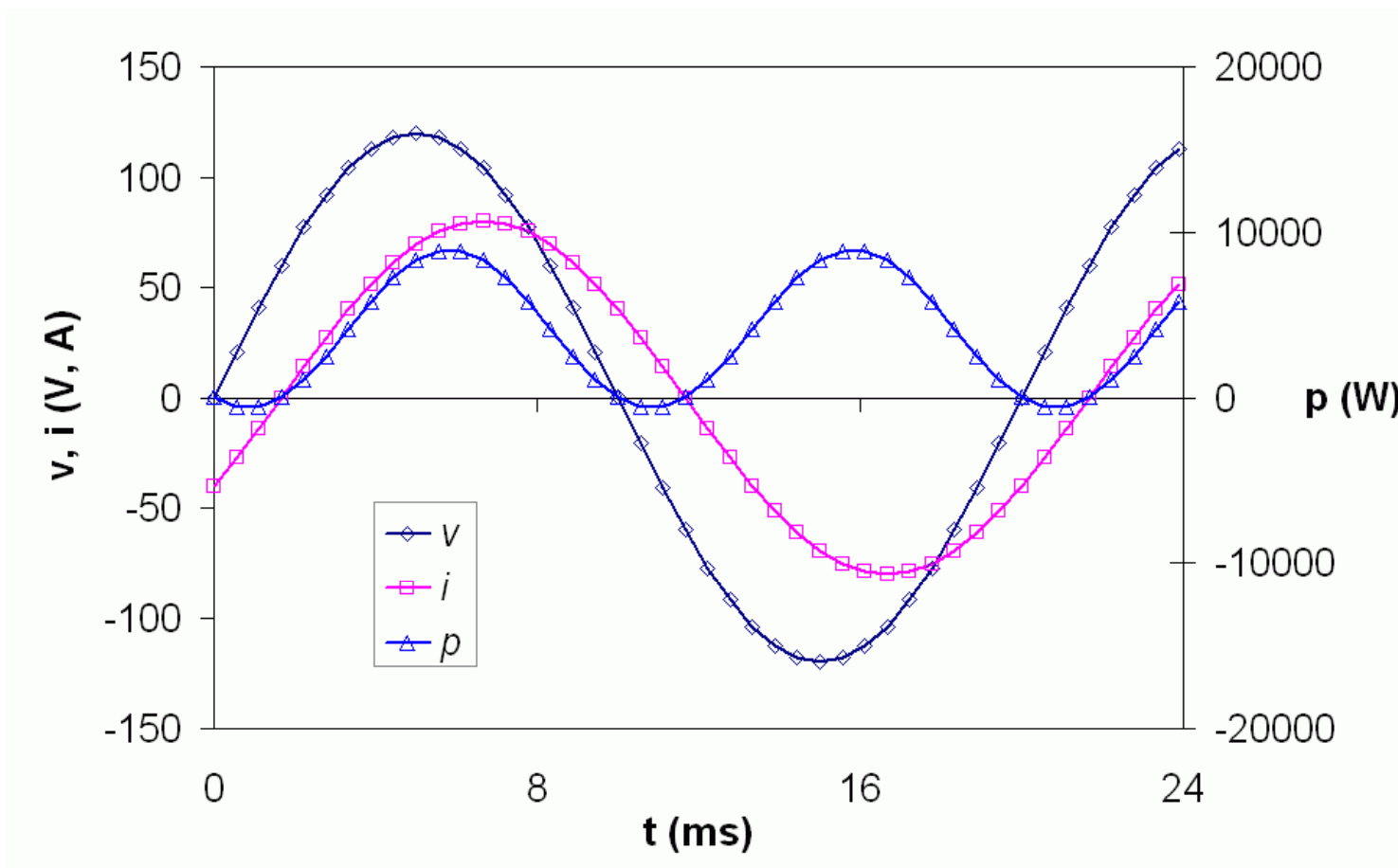

- single phase systems:
  - have large and undesirable fluctuations in instantaneous power


Three phase:

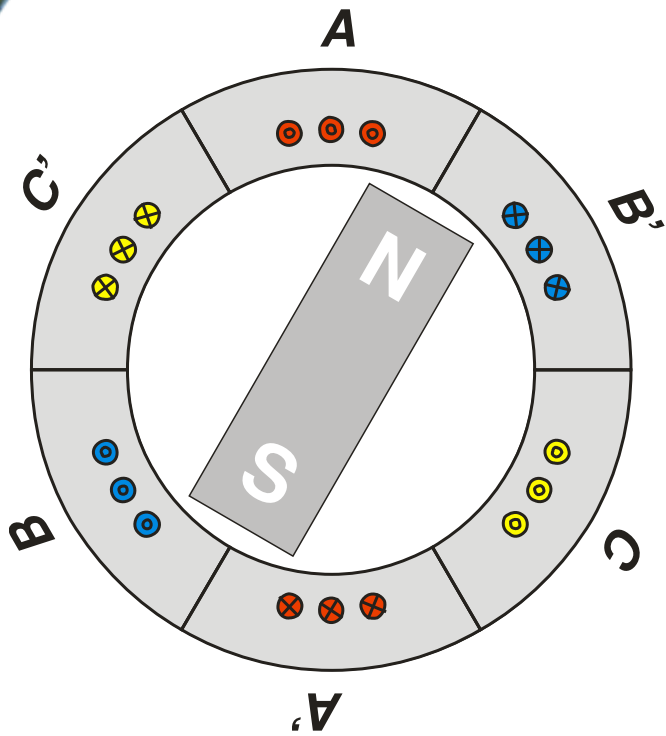

$$v_A = V_m \sin \omega t$$

$$v_B = V_m \sin(\omega t - 120^\circ)$$

$$v_C = V_m \sin(\omega t - 240^\circ)$$

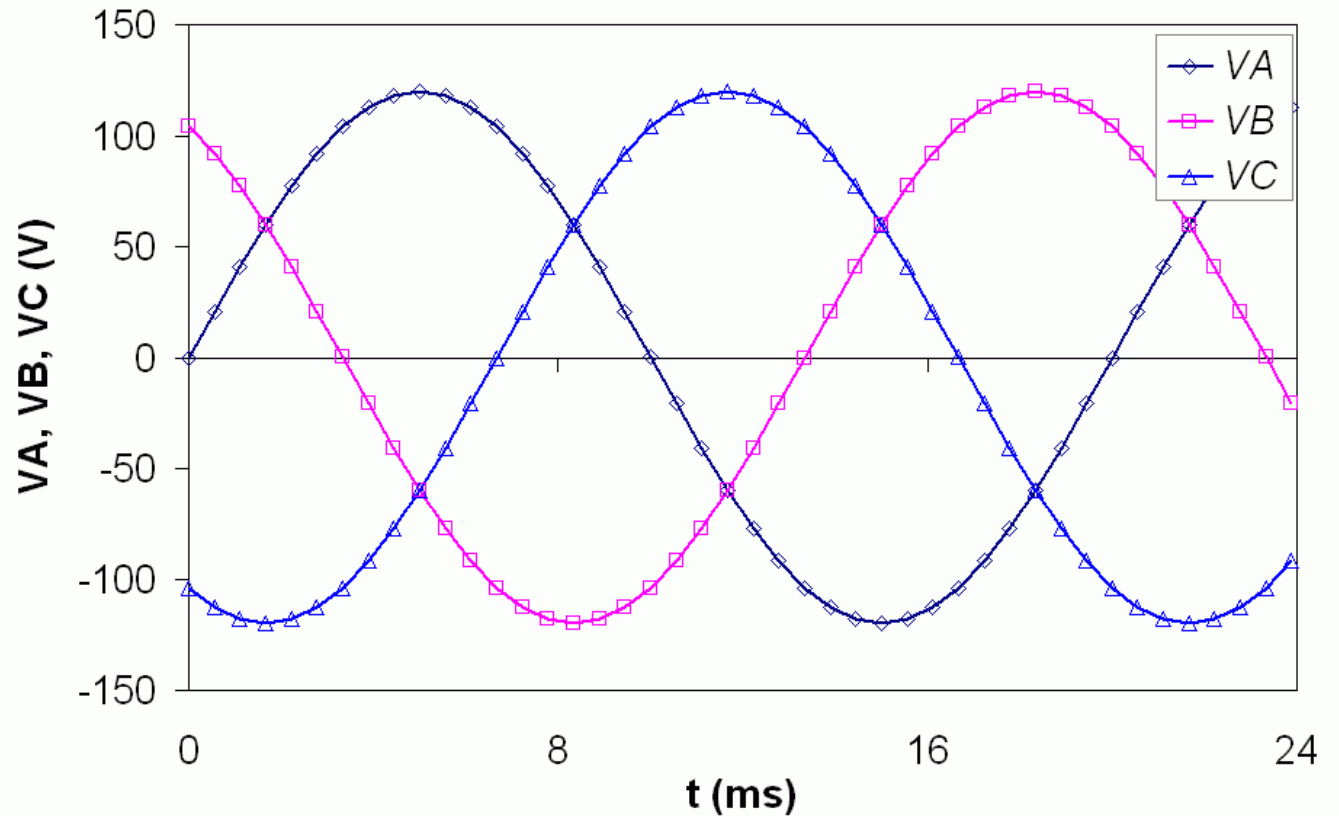



power for phase **A**

$$P_A = VI \cos \phi - VI \cos(2\omega t - \phi)$$

power for phase **B**

$$P_B = VI \cos \phi - VI \cos(2\omega t - \phi - 240^\circ)$$

power for phase **C**

$$P_C = VI \cos \phi - VI \cos(2\omega t - \phi - 480^\circ)$$




total instantaneous power

$$\begin{aligned}P &= P_A + P_B + P_C \\&= 3VI \cos \phi - VI \left[ \cos(2\omega t - \phi) + 2 \cos(2\omega t - \phi - 180^\circ) \cos 60^\circ \right] \\&= 3VI \cos \phi - VI \left[ \cos(2\omega t - \phi) - \cos(2\omega t - \phi) \right] \\&= 3VI \cos \phi - 0\end{aligned}$$

$$P = 3VI \cos \phi$$

Prime mover

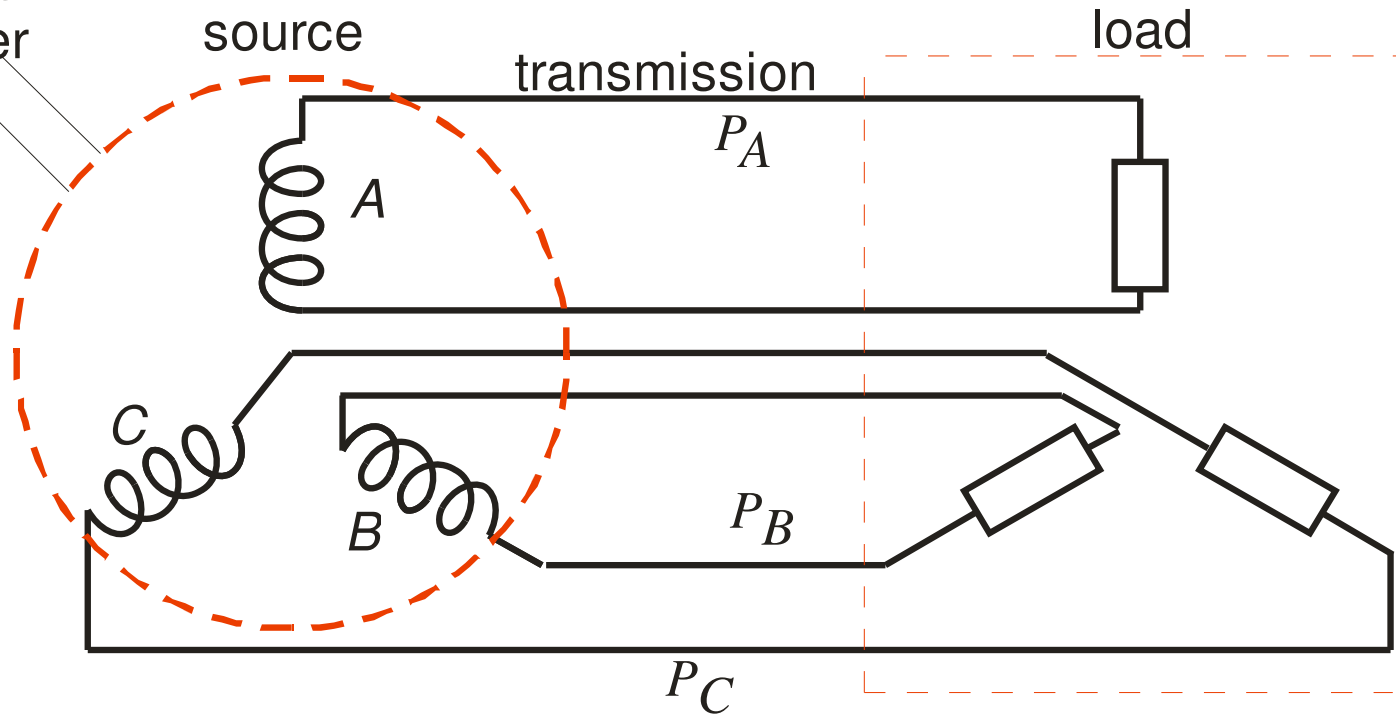



- advantage 1:

- power from the prime mover to the load is absolutely constant
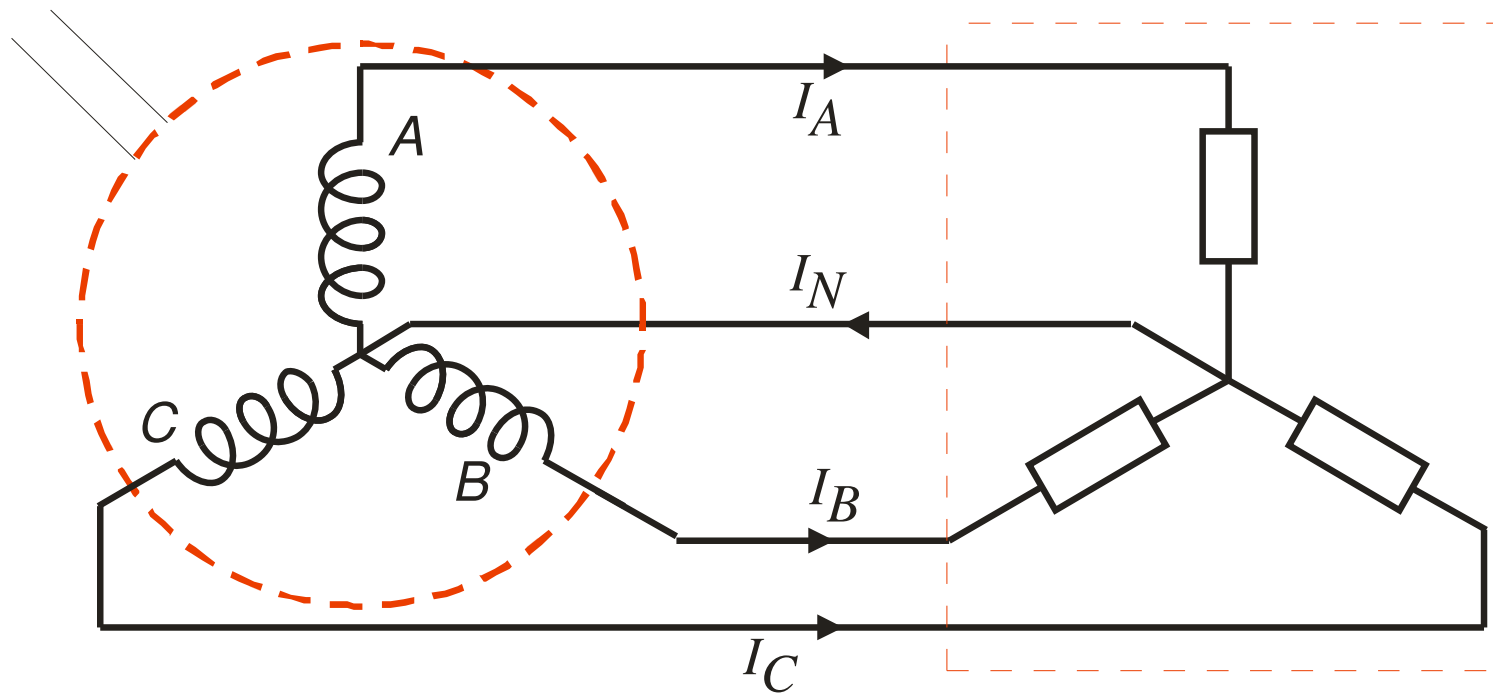
## Three phase transmission:

- instead of 6 conductors between the generator and load,
- join the windings together as shown and have 4 conductors



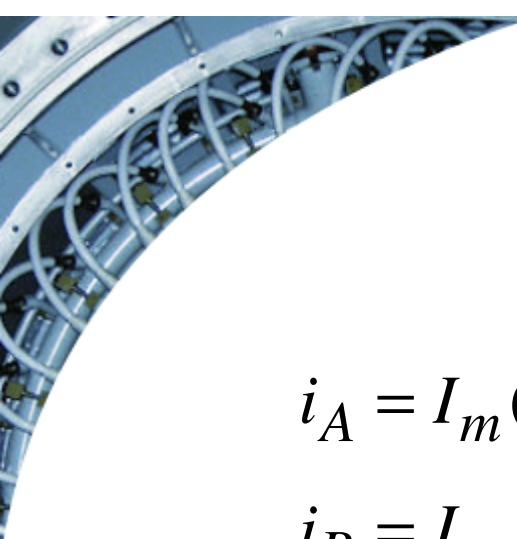
$$i_A = I_m (\sin \omega t - \phi)$$

$$i_B = I_m \sin(\omega t - \phi - 120^\circ)$$

$$i_C = I_m \sin(\omega t - \phi - 240^\circ)$$

$$i_N = i_A + i_B + i_C$$




$$= I_m \left[ \sin(\omega t - \phi) + 2 \sin(\omega t - \phi) \cos 120^\circ \right]$$


$$= 0$$




- current in the **neutral** conductor under balanced conditions is **zero**
- we need only have **3** conductors for our three-phase system
  
- **advantage 2:**
  - there is a big saving in transmission conductors

# Space factor of machines

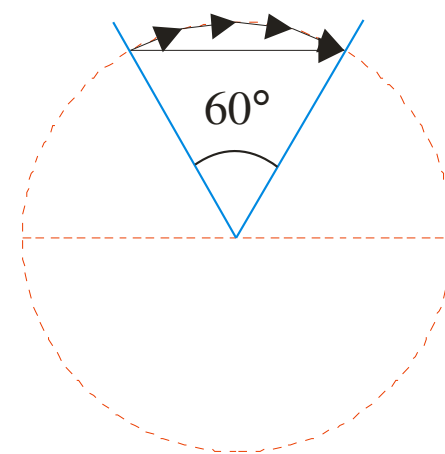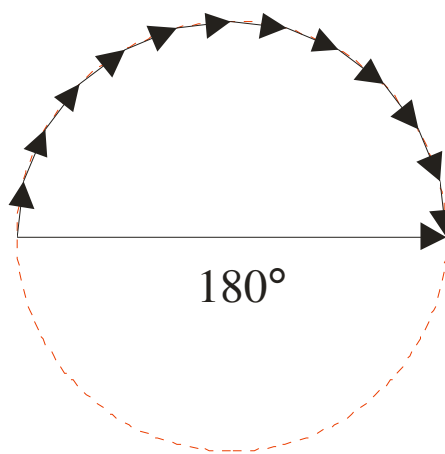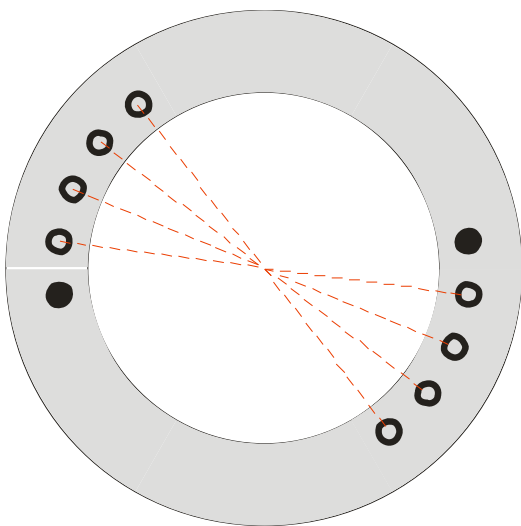

- 
- if stator of the generator is wound for 3 separate phases instead of just one single phase,
    - we obtain a higher value of distribution factor
    - the result of this is that there is bigger value of space factor
  - **advantage 3:**
    - output per unit volume of three phase machines is higher than for single phase machines

# 7.4 3-phase power systems

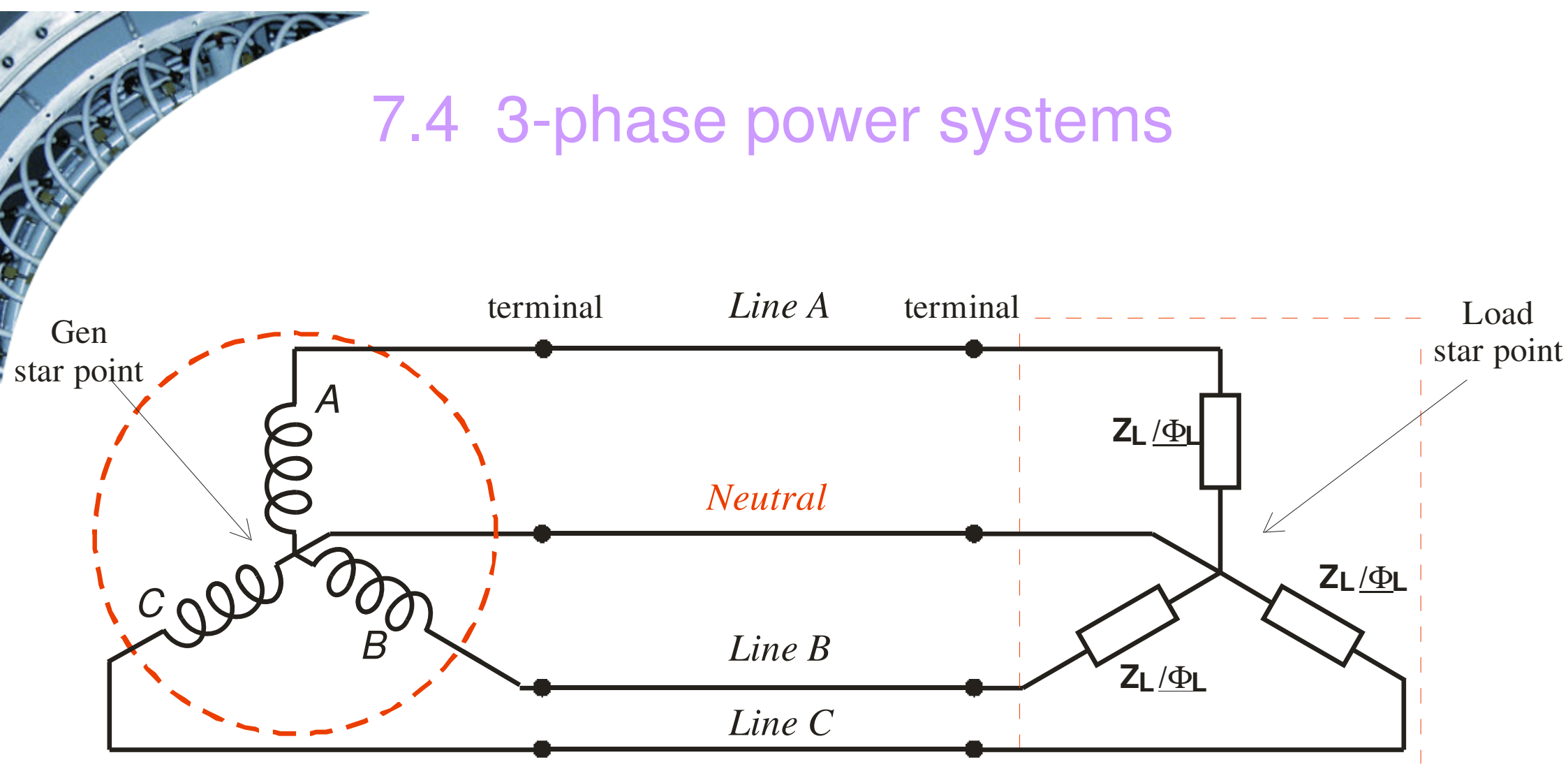

- 
- **balanced supply:**
    - same magnitude of voltage every  $120^\circ$

$$V_A = V_p \underline{/0^\circ}$$

$$V_B = V_p \underline{/120^\circ}$$

$$V_C = V_p \underline{/240^\circ}$$



- balanced load

- same impedance in each phase every  $120^\circ$

- same magnitude and phase



- $\overline{Z_L} = Z_L / \phi$

- this is normal for large 3-phase loads,

- not so for individual single-phase loads


- 
- **balanced system**
    - both supply and load are balanced
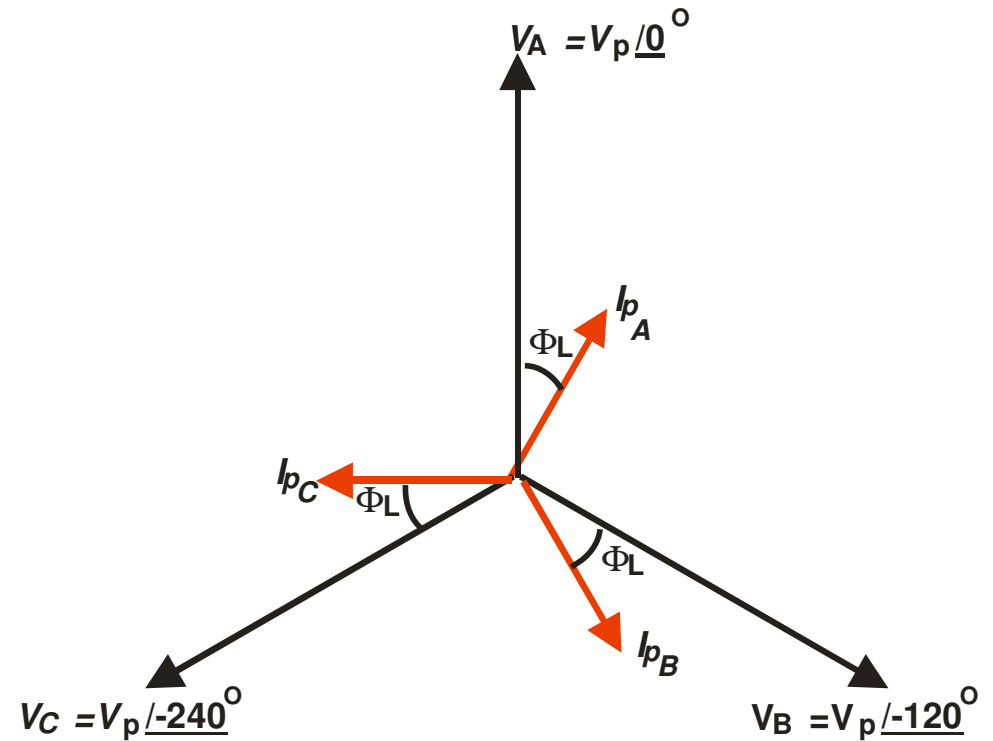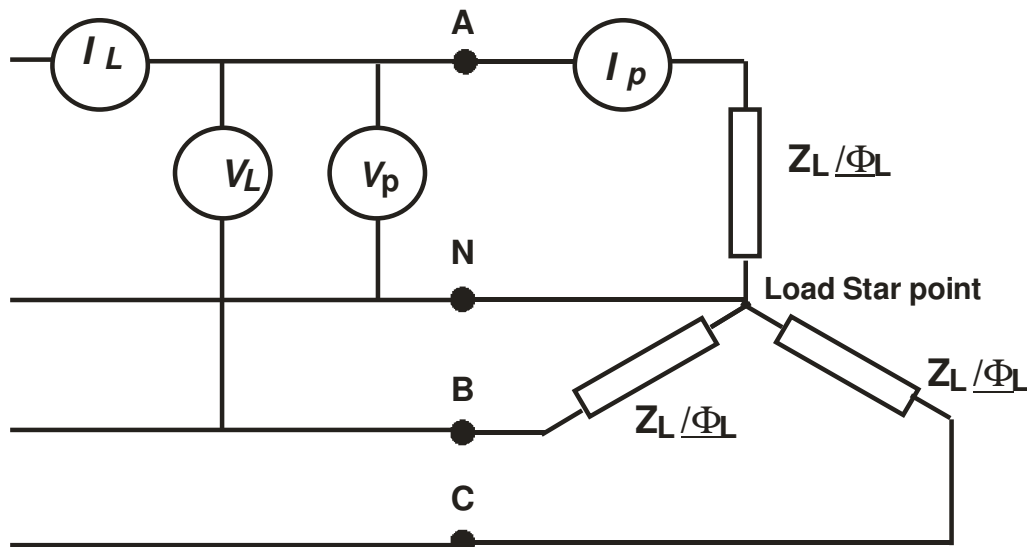
## 7.4.1 balanced system star-connected load



- subscript  $p$ : phase,
  - means looking at one phase
- subscript  $L$ : line,
  - means looking at three phases

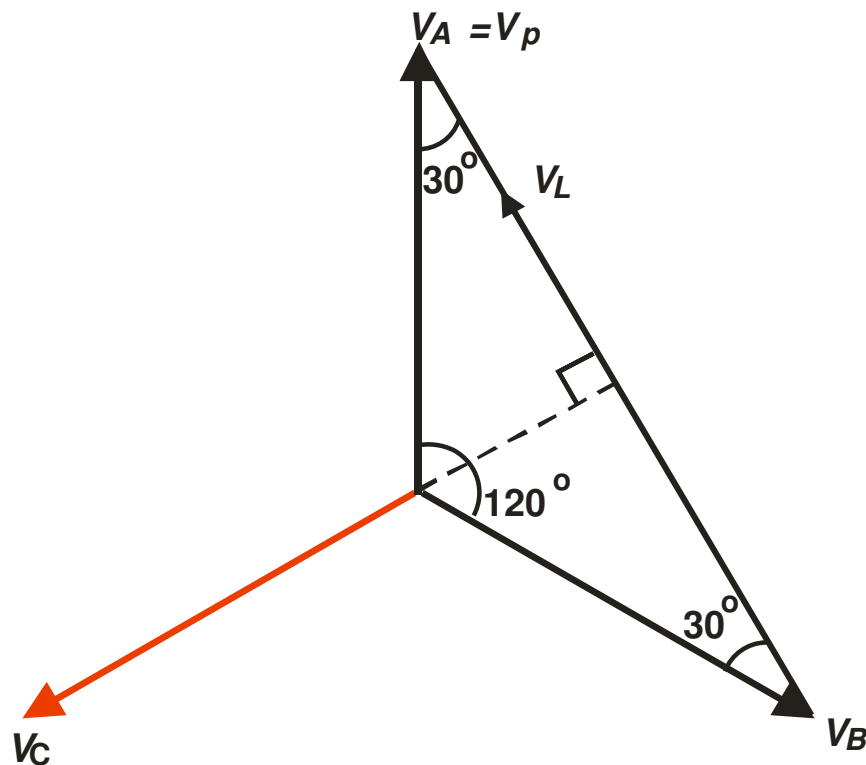- A balanced supply voltage applied to a balanced load gives
  - a balanced set of phase currents
    - same magnitude and displaced every  $120^\circ$



$$\frac{V_L}{2} = V_p \cos 30^\circ$$

$$V_L = \sqrt{3}V_p$$

$$I_L = I_p$$

- 
- Power in one phase

$$P_p = V_p I_p \cos \phi_L$$

$V_p$ : phase voltage magnitude


$I_p$ : phase current magnitude

$\phi_L$ : angle between  $V_p$  and  $I_p$

- Total power in three phase


$$P_T = 3P_p = 3V_p I_p \cos \phi_L = \sqrt{3} V_L I_L \cos \phi_L$$
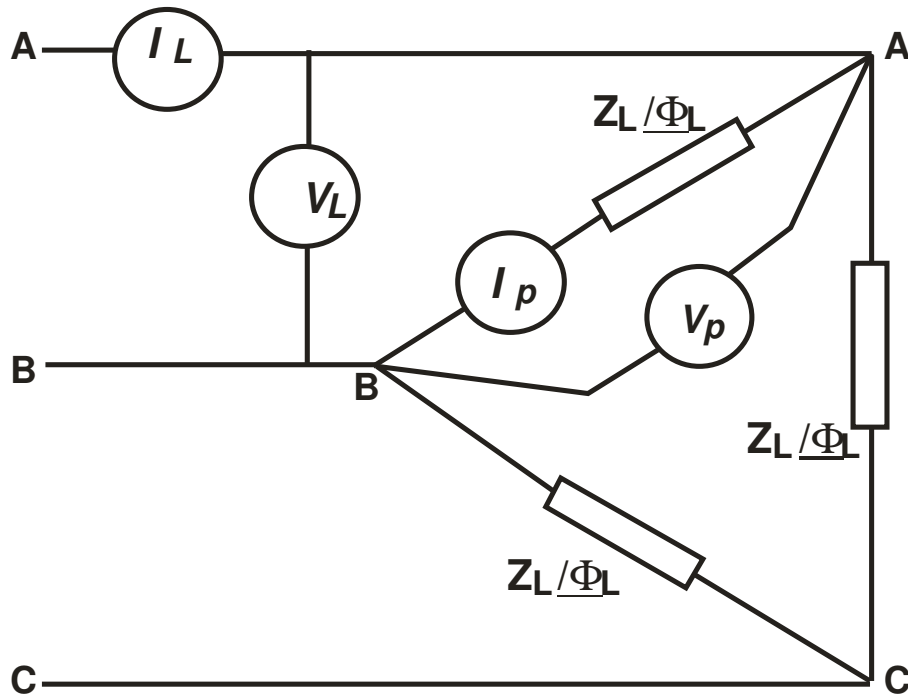
## 7.4.2 balanced system delta-connected load




$$V_L = V_p$$

$$I_L = \sqrt{3}I_p$$


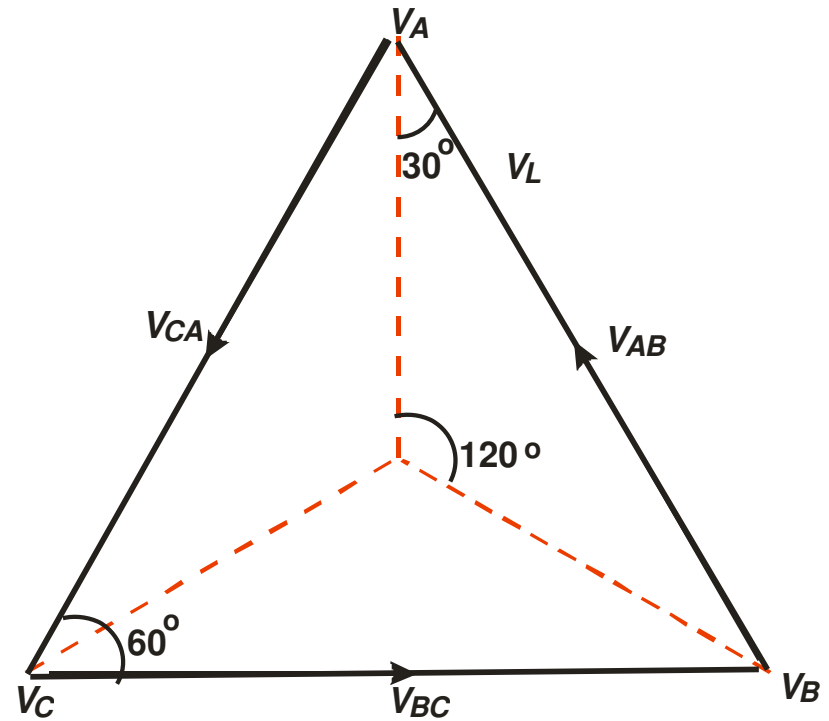


$$\bar{I}_A = \bar{I}_{AB} - \bar{I}_{CA}$$

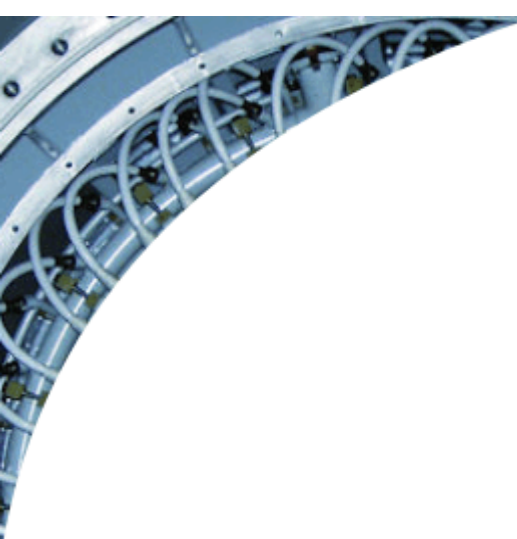
$$P_p = V_p I_p \cos \phi_L$$


$$P_T = 3P_p = 3V_p I_p \cos \phi_L = \sqrt{3} V_L I_L \cos \phi_L$$
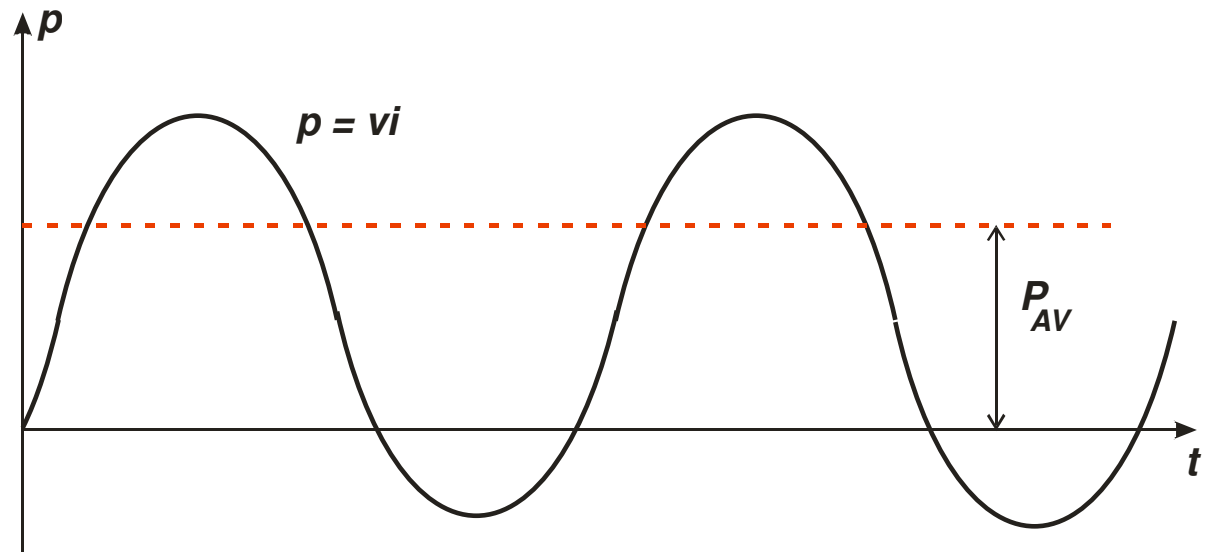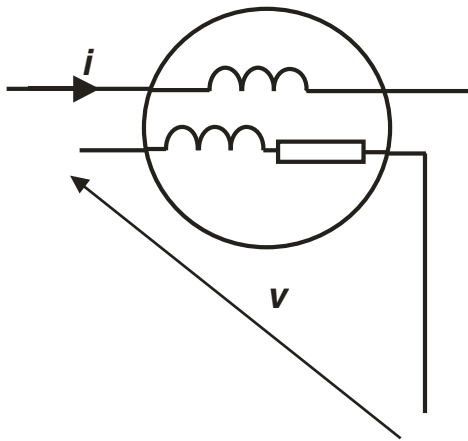
# 7.5 Measurement of Power in 3-phase Systems



- Wattmeter responds to average power

$$P_{AV} = vi|_{AV}$$

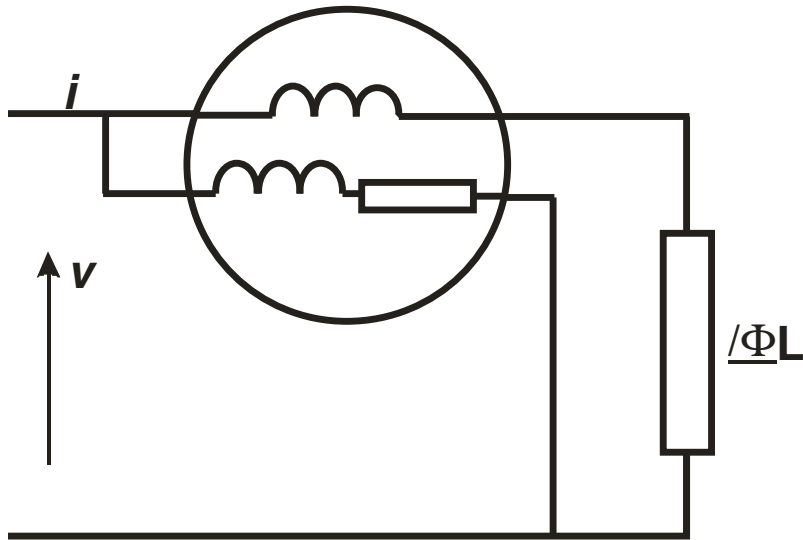

In this circuit

$$P_{AV} = vi|_{AV} = "VI \cos \phi_L "$$

where


$V$ : rms voltage at terminal of meter

$I$ : rms current into meter

$\phi_L$ : angle between  $V$  and  $I$  supplied to the meter

## 7.5.1. One-wattmeter method

- With a balanced load

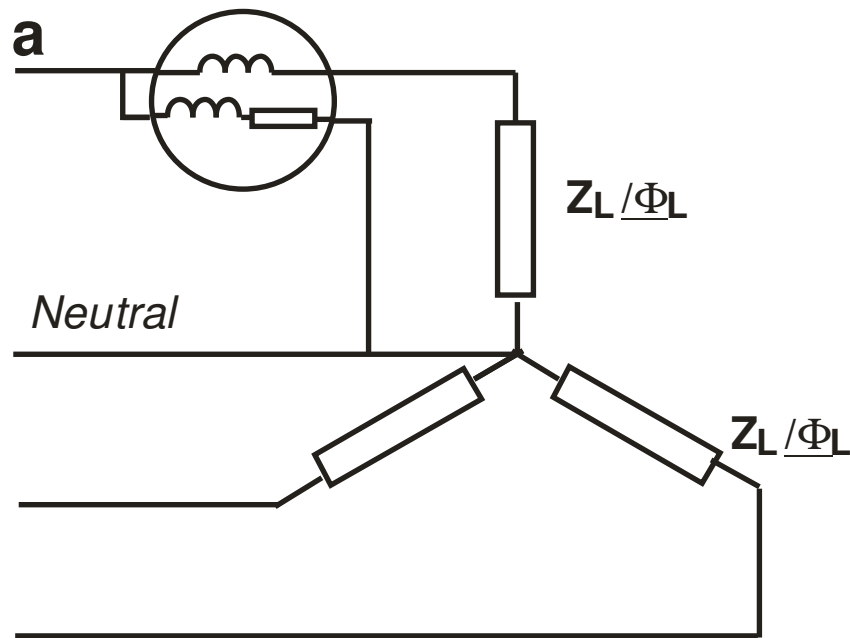

$$\text{"Reading"} = "VI \cos \phi_L"$$
$$= V_p I_p \cos \phi_L$$

power in one phase


$$P_p = V_p I_p \cos \phi_L$$

total power

$$P_T = 3P_p$$
$$= 3V_p I_p \cos \phi_L$$



$$P_T = 3 \times \text{"meter reading"}$$

## 7.5.2 Two-wattmeter method

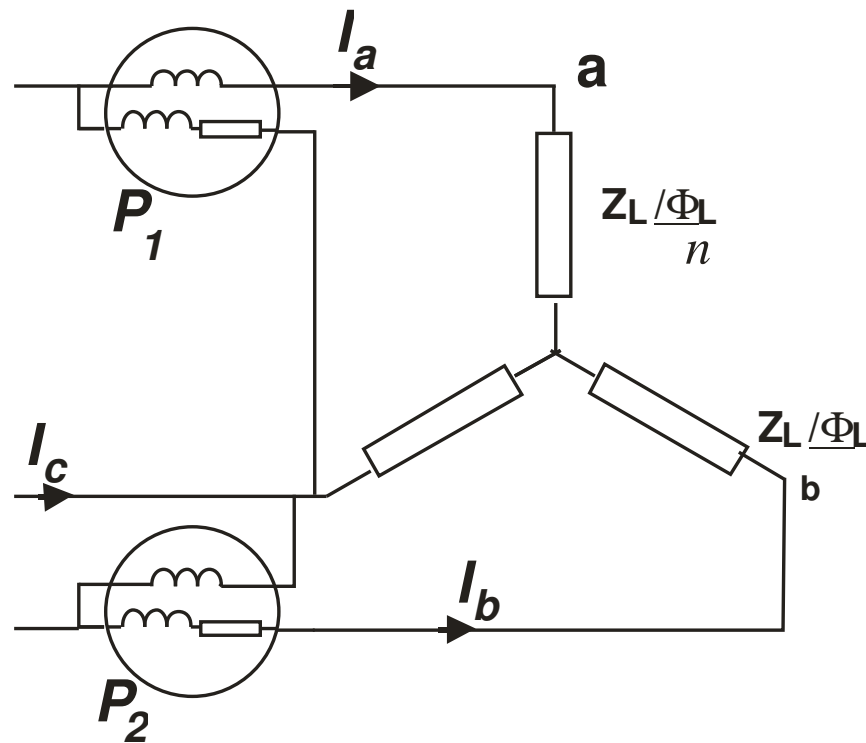

- connection:

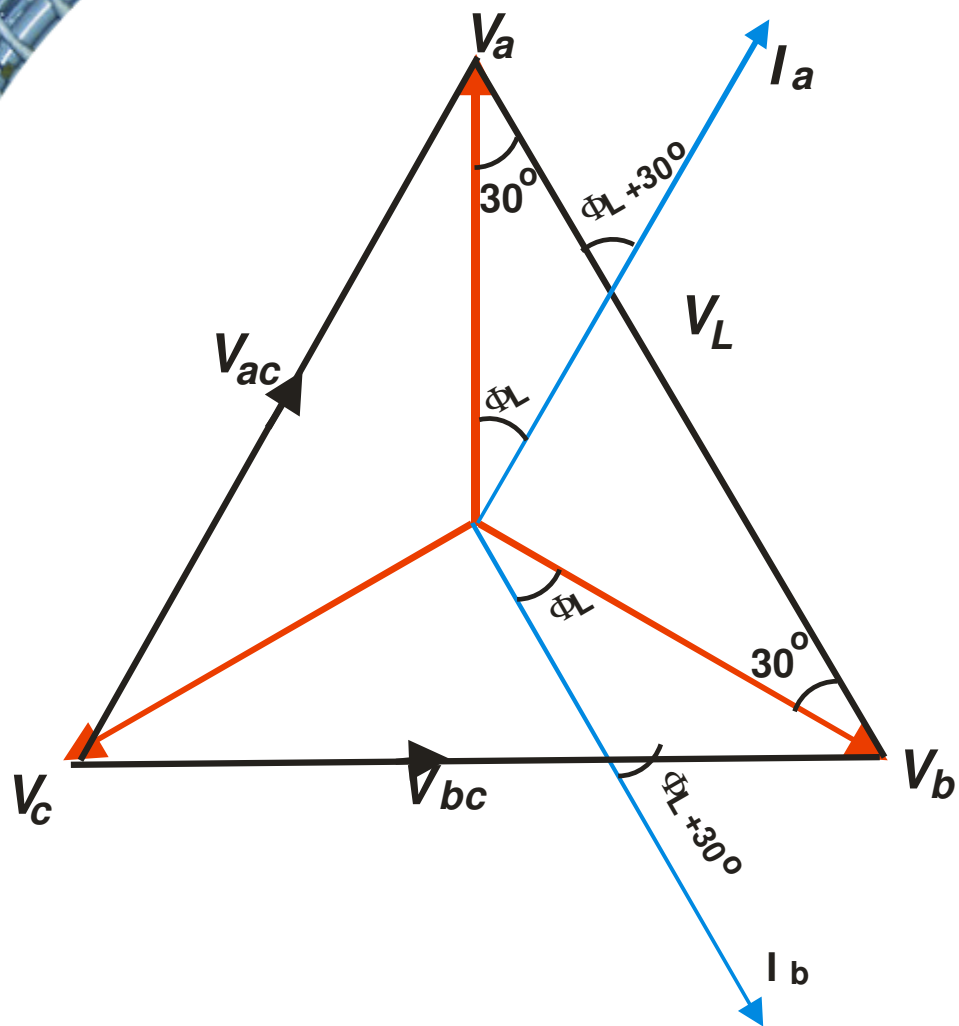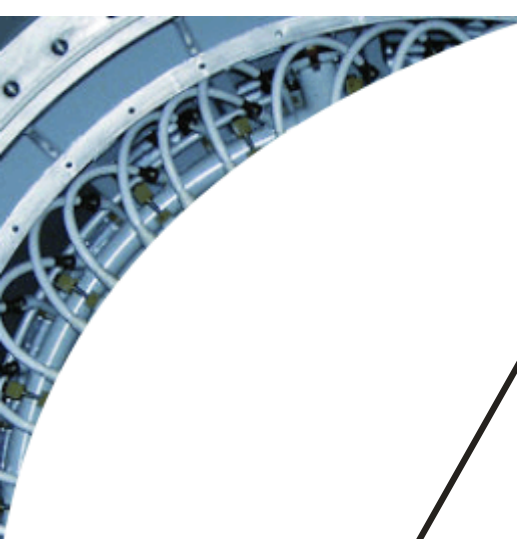- current coil of  $P_1$  and  $P_2$  in any two of the phases
- negative of voltage coil of  $P_1$  and  $P_2$  both connected to the 3rd phase



## Meter Readings:

$$P_1 = "VI \cos \phi" = V_{ac} I_a \cos(\phi_L - 30^\circ)$$

$$P_2 = "VI \cos \phi" = V_{bc} I_b \cos(\phi_L + 30^\circ)$$

$$P_1 = V_L I_L \cos(\phi_L - 30^\circ)$$

$$P_2 = V_L I_L \cos(\phi_L + 30^\circ)$$



Power:

$$P_1 + P_2 = V_L I_L \left[ \cos(\phi_L - 30^\circ) + \cos(\phi_L + 30^\circ) \right]$$

$$P_1 + P_2 = V_L I_L 2 \cos \phi_L \cos 30^\circ$$

$$P_1 + P_2 = \sqrt{3} V_L I_L \cos \phi_L$$

$$P_1 + P_2 = \text{Total Power}$$

## Power Factor:

$$\begin{aligned}P_1 - P_2 &= V_L I_L \left[ \cos(\phi_L - 30^\circ) - \cos(\phi_L + 30^\circ) \right] \\&= V_L I_L 2 \sin \phi_L \sin 30^\circ \\&= V_L I_L \sin \phi_L\end{aligned}$$

$$\frac{P_1 - P_2}{P_1 + P_2} = \frac{V_L I_L \sin \phi_L}{\sqrt{3} V_L I_L \cos \phi_L} = \frac{1}{\sqrt{3}} \tan \phi_L$$


$$\text{Power factor} = \cos \phi_L$$



- **Advantages of two-wattmeter method:**

- neutral is not required, eg neutral may be buried in motor
- from the two meter readings both total power and power factor can be determined
- method is valid even for unbalanced situations,
  - ie total power is equal to the sum of the readings

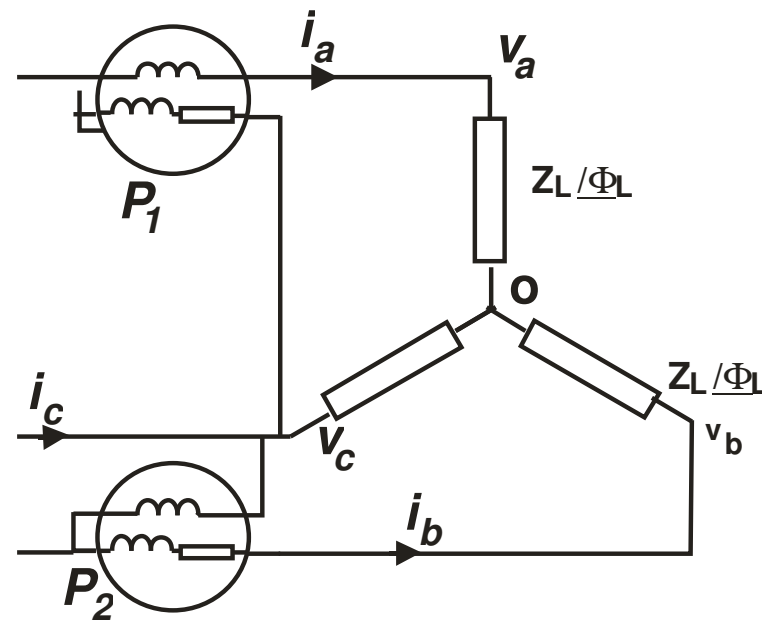To show that  $P_1 + P_2 = P_T$  even for unbalanced situations



$$P_1 = (v_{ac} i_a) \Big|_{AV} = (v_a - v_b) i_a \Big|_{AV}$$

$$P_2 = (v_{bc} i_b) \Big|_{AV} = (v_b - v_c) i_b \Big|_{AV}$$

$$P_1 + P_2 = (v_a i_a) \Big|_{AV} + (v_b i_b) \Big|_{AV} - v_c (i_a + i_b) \Big|_{AV}$$

- 
- if there is no neutral


$$i_a + i_b + i_c = 0$$

- therefore

$$P_1 + P_2 = (v_a i_a) \Big|_{AV} + (v_b i_b) \Big|_{AV} + (v_c i_c) \Big|_{AV}$$

$$P_1 + P_2 = P_a + P_b + P_c$$
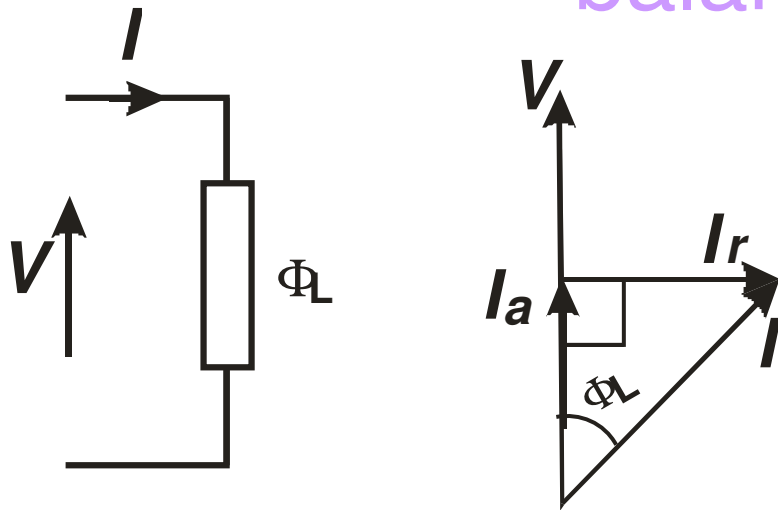
## 7.5.3 Measurement of reactive power in 3-ph balanced system





$$\text{Active power} = P = VI \cos \phi_L = VI_a \quad [\text{W}] \quad (\text{real power})$$

$$\text{Reactive power} = Q = VI \sin \phi_L = VI_r \quad [\text{VAr}] \quad (\text{imaginary power})$$

$$\text{Apparent power} = S = VI = VI \quad [\text{VA}] \quad (\text{complex power})$$
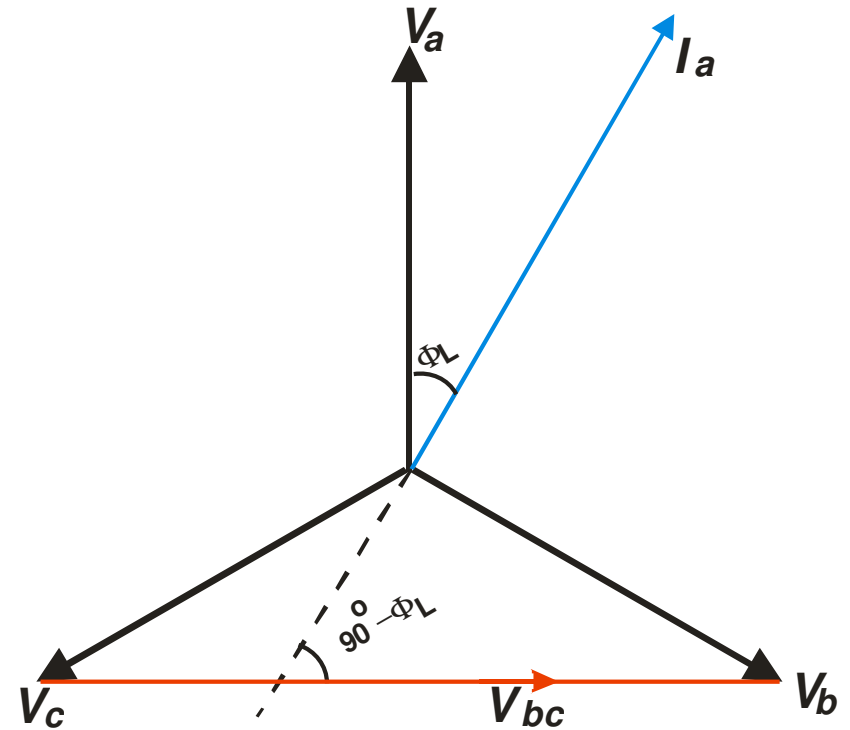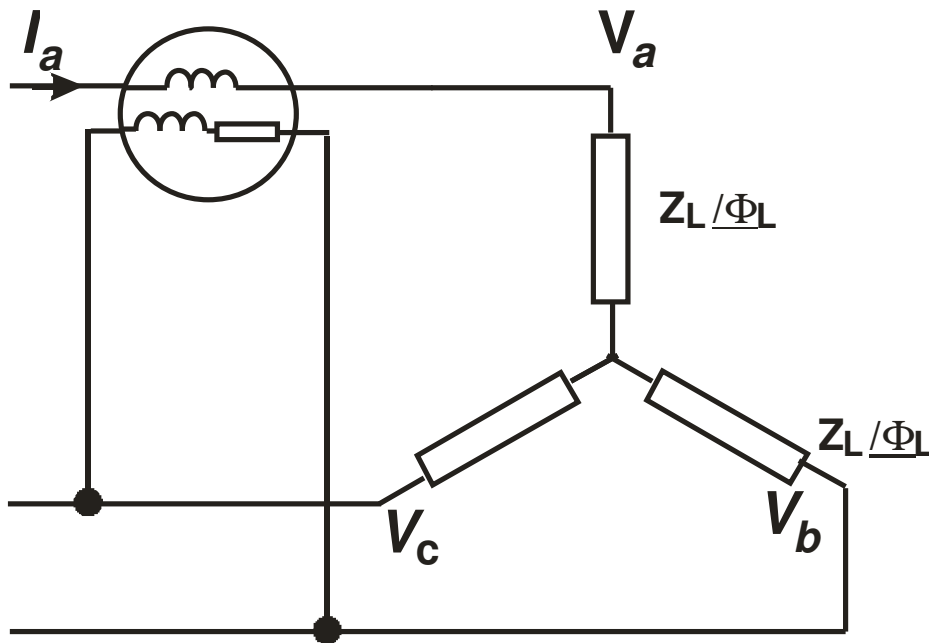
## Connection for reactive power measurement



- current coil in one phase
- voltage coil across the other two phases



Meter reading:

$$\begin{aligned} "VI \cos \phi" &= V_{bc} I_a \cos(90^\circ - \phi_L) \\ &= V_L I_L \sin \phi_L \end{aligned}$$

Reactive power in one phase:

$$= V_p I_p \sin \phi_L$$

Total reactive power:

$$\begin{aligned} Q_T &= 3V_p I_p \sin \phi_L \\ &= \sqrt{3} V_L I_L \sin \phi_L \\ &= \sqrt{3} \times \text{Wattmeter Reading} \end{aligned}$$



## Examples 7

1)

A 3-phase 50-Hz supply has a load comprising three similar coils connected to it in star. The line current is 20 A, with associated input apparent power of 20 kVA and active power of 11 kW.

Determine

a) the line and phase voltages

b) the input reactive power

c) the resistance and inductance of the coil.

If the coils are connected in delta to the same supply, find

d) the line current


e) the active power.



2)

Each phase of a delta connected load consists of a resistor  $R$  and a capacitor  $C$  in parallel. When connected to a balanced 3-phase supply the “two-wattmeter” method gave readings of 1000 W and 500 W, the line voltage being 400 V, 50 Hz and the line current being 2.5 A.

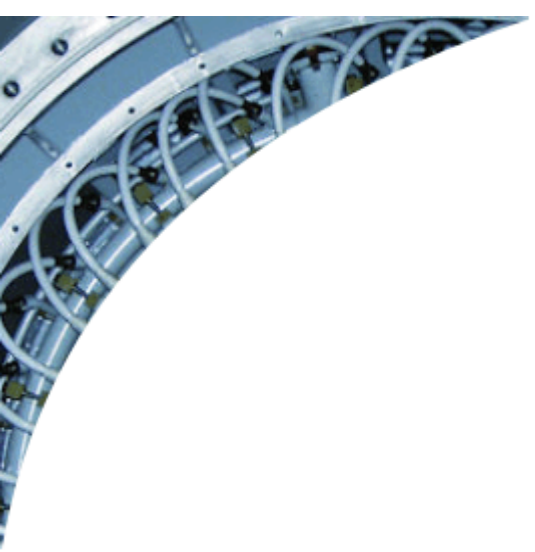- a) Calculate the load power factor using the total power, voltage and current
- b) Calculate the load power factor using the two wattmeter readings only
- c) Determine the values of  $R$  and  $C$ .



- End of Lecture 7 -