

**MEC 3102 – PRODUCTION
ENGINEERING I AND
ELECTRICITY & ELECTRONICS II
Department of Mechanical Engineering**

Name: Mr. Munkombwe Boyd,

Old School of Engineering Bldg.,

Cell: 0968315273/0950435239

Email: boyd.munkombwe@unza.zm

2nd Series Assignment [2]

1. **You are tasked** to choose an appropriate method of electric power generation. What factor do you need to consider before presenting you best method?[10]
2. **What are the** conventional and alternative methods of energy sources? [6]
3. What are the advantages and disadvantages of nuclear energy generation?[6]
4. **In a nuclear power** generation, explain the importance of the control rods?[4]
5. What are the disadvantages of conventional methods of power generation?[2]
6. What is a power system?[2]
7. **Differentiate between** Primary and Secondary power distribution. [2]
8. What are the advantages and disadvantage of A.C. power transmission? [6]
9. **A three-phase delta-**connected load, each phase of which has an inductive reactance of $40\ \Omega$ and a resistance of $25\ \Omega$, is fed from the secondary of a three-phase star-connected transformer which has a phase voltage of 230 V. Draw the circuit diagram of the system and calculate: [12]
 - (a) The current in each phase of the load;
 - (b) The p.d across each phase of the load;
 - (c) The current in the transformer secondary windings;
 - (d) The total active power taken from the supply and its power factor
10. Non-reactive loads of 10, 6 and 4 kW are connected between the neutral and the red, yellow and blue phases respectively of a three-phase, four-wire system. The line voltage is 400 V. Find the current in each line conductor and in the neutral.[10]
11. **Each phase of star** connected load consists of non-inductive resistance of $50\ \Omega$ in parallel with a capacitance of $63.6\ \mu\text{F}$. Calculate:
 - i. The line current,
 - ii. Total power absorbed,
 - iii. Total kVA and
 - iv. The power factor when this load is connected to a 381 V (line voltage), 3-phase, 50Hz supply.

12. Three similar coils, connected in star, take a total power of 1.5 kW, at a power factor of 0.2, from a three-phase, 400 V, 50 Hz supply. Calculate:
- The resistance and inductance of each coil;
 - the line currents if one of the coils is short-circuited.
13. Two wattmeters are used for measuring the power input and the power factor of an over-excited synchronous motor. If the reading of the meters are (-2.0 kW) and (+7.0 kW) respectively. Calculate the input power and power factor of the motor.

NOTE: This assignment is due on the **06/08/2021**

Write your answers clearly for the highlighted questions and send scans/pictures of your answers.